

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-IV (NEW) - EXAMINATION – SUMMER 2018

Subject Code:2141002

Date:17/05/2018

Subject Name:Analog Circuit Design

Time:10:30 AM to 01:00 PM

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Define the following parameters of Op-Amp: **03**
(i) Slew Rate
(ii) Common Mode Rejection Ratio.
(iii) PSRR
- (b) Draw Hybrid - π equivalent circuit for CE transistor. Also derive the equation of transconductance g_m . **04**
- (c) Explain application of op-amp (Inverting configuration) as summing, scaling and averaging circuit. **07**
- Q.2** (a) Sketch equivalent circuit of crystal and discuss its application in oscillator circuit. Draw crystal based oscillator circuit. **03**
- (b) Design RC phase oscillator for the frequency of 3KHz. **04**
- (c) What is an oscillator? Explain the concept of oscillation with Barkhausen criteria. **07**
- OR**
- (c) Draw op-amp based Wien-bridge oscillator circuit and obtain its frequency of oscillation. **07**
- Q.3** (a) List out characteristics of ideal op-amp. **03**
- (b) Draw BJT based emitter coupled differential amplifier circuit. How can we improve its CMMR? **04**
- (c) Draw peaking amplifier. Specify the value of all components to provide a gain of 10 at a peak frequency of 16 KHz. Take $L = 10\text{mH}$ with internal resistance of 30Ω . **07**
- OR**
- Q.3** (a) What are the problems associated with op-amp based basic differentiator circuit? Suggest possible solution. **03**
- (b) Explain the requirement of Instrumentation amplifier. **04**
- (c) Explain the operation of op-amp based sample and hold circuit and state its application. **07**
- Q.4** (a) What is thermal drift? How does it affect the performance of an op-amp circuit? **03**
- (b) Define and explain the 'Lock range' and 'Capture range'. **04**
- (c) Design a free running ramp generator using IC 555 for $V_{cc}=10\text{V}$, $C=0.1\mu\text{F}$ and period $T = 2\text{ms}$. Take transistor with $\beta = 100$. Explain its working. **07**
- OR**
- Q.4** (a) What do you understand by precision rectifier? Draw half wave precision rectifier circuit. **03**
- (b) Sketch the circuit of FM detector using PLL and explain its working. **04**
- (c) Design an astable multivibrator using IC555 with repetition frequency of 1KHz and duty cycle 70%. Assume $C=0.1\mu\text{F}$. Draw designed Circuit and waveforms. **07**
- Q.5** (a) Explain zero crossing detector with circuit diagram and waveforms. **03**

- (b) State the advantages and disadvantages of SMPS. **04**
- (c) Design a Delyiannis-Friend circuit with $f_0 = 12.5\text{KHz}$, $Q=10$ and mid band gain $H = 26\text{dB}$. **07**

OR

- Q.5** (a) Discuss magnitude scaling and frequency scaling in filter design. **03**
- (b) Comparison of linear and switching mode regulators. **04**
- (c) Design a 1.5KHz low pass second order Butterworth filter, Use the Sallen and Key equal component model. Assume the damping factor to be $\sqrt{2}$. **07**
