

Seat No.: \_\_\_\_\_

Enrolment No. \_\_\_\_\_

**GUJARAT TECHNOLOGICAL UNIVERSITY**

**BE - SEMESTER-IV (NEW) - EXAMINATION – SUMMER 2018**

**Subject Code:2142405**

**Date:19/05/2018**

**Subject Name:Analog Electronics and Its Applications**

**Time:10:30 AM to 01:00 PM**

**Total Marks: 70**

**Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) What are the significances of DC load line characteristics? **03**  
(b) Draw and explain the equivalent circuit of OPAMP. **04**  
(c) Discuss application of diode as half wave rectifier with filter for resistive load. **07**  
Draw necessary waveforms and figures.
- Q.2** (a) Draw the hybrid-pi model for a transistor in CE configuration. **03**  
(b) Draw and explain input and output characteristic of CC configuration of BJT. **04**  
(c) Define: (1) CMRR (2) Input offset voltage (3) Slew rate (4) Input bias current **07**  
(5) PSRR (6) Thermal drift (7) Bandwidth
- OR**
- (c) Explain class AB amplifier along with necessary figures, waveforms and applications. **07**
- Q.3** (a) Discuss the block diagram of OPAMP. **03**  
(b) Explain the series voltage regulator with foldback current limiting circuit. **04**  
(c) Explain inverting type summing amplifier having three input voltage source. **07**
- OR**
- Q.3** (a) Draw and explain V to I converter with floating load. **03**  
(b) Explain square wave generator with diagram. **04**  
(c) Explain ideal integrator and derive the output voltage equation. **07**
- Q.4** (a) Explain the principal of oscillator. **03**  
(b) Discuss zero crossing detector circuit. **04**  
(c) Brief switched capacitor circuit and explain MF5 switched capacitor filter. **07**
- OR**
- Q.4** (a) Differentiate active and passive filter. **03**  
(b) Explain the frequency response of high pass filter. **04**  
(c) Discuss wien bridge oscillator with necessary diagram and waveform. **07**
- Q.5** (a) Compare TTL and RTL. **03**  
(b) Draw the constructional diagram of AND gate, OR gate, NOT gate using discrete components like diode, resistor, transistor etc. **04**

(c) Explain with neat sketches F/V converter. **07**

**OR**

**Q.5** (a) Draw the diagram of first and second order butterworth filter. **03**

(b) Explain the block diagram of V/F converter. **04**

(c) Discuss the monostable mode of 555 timer with necessary diagram and waveform. **07**

\*\*\*\*\*