

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-IV (NEW) - EXAMINATION – SUMMER 2018

Subject Code:2142406

Date:24/05/2018

Subject Name:Digital Electronics and its applications

Time:10:30 AM to 01:00 PM

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain D’Morgans theorem with truth table. **03**
(b) Fill in the blanks. **04**
(1) $(105.25)_{10} = (\quad)_2$
(2) $(0111001.010)_8 = (\quad)_{16}$
(c) Explain NOR as universal gate. **07**
- Q.2** (a) Minimize following function. **03**
 $AB + A'C + BC$
(b) Draw five variable K-map. **04**
(c) $f(A,B,C,D) = f = \Sigma m(1,2,3,5,7,11,13)$ Minimize this function using K-map. **07**
And draw logic diagram for the function.
- OR**
- (c) Plot the following expression on a Karnaugh map. **07**
 $Z = (A \cdot B) \odot (C + D).$
- Q.3** (a) Define Fan in and Fan out for digital circuits. **03**
(b) Define ROM, PROM, EPROM, EEPROM. **04**
(c) Explain full subtractor and derive its digital logic. **07**
- OR**
- Q.3** (a) Explain encoder with example. **03**
(b) Explain D-multiplexer as distributor. **04**
(c) Construct full adder circuit by 3 to 8 decoder. **07**
- Q.4** (a) What is edge-triggered flip-flop? **03**
(b) Explain R-S flip flop. **04**
(c) Explain Master Slave J-K flip flop. **07**
- OR**
- Q.4** (a) What we mean by don't care condition ? **03**
(b) Define shift registers. Also list its types. **04**
(c) Design a logic circuit to convert the BCD code to Excess – 3 code. **07**
- Q.5** (a) Using 10's complement, subtract : $(72532-3250)_{10}$ **03**
(b) What is race around condition? **04**
(c) Explain the working of BCD Ripple Counter with the help of state diagram and logic diagram. **07**
- OR**
- Q.5** (a) Explain D-flip flop in brief. **03**
(b) Give the comparison between synchronous & Asynchronous counters. **04**
(c) Design and explain 3 bit data comparator circuit. **07**
