

GUJARAT TECHNOLOGICAL UNIVERSITY**BE (SPFU)- SEMESTER- 1st/ 2nd • EXAMINATION – 2018****Subject Code: ENG005****Date: 28-05-2018****Subject Name: Linear Electrical Networks****Time: 02.30 PM to 05.00 PM****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain Star delta transformation with example. **07**
(b) Explain Norton's theorem. **07**
or
(b) Explain Thevenin's theorem.
- Q.2** (a) Explain Kirchhoff's current and voltage law. **07**
(b) Explain series and parallel connection. Also compare them. **07**
- Q.3** (a) What is resistor? How to calculate the resistor value by color code? **07**
(b) Explain loop, node, path, network and circuit **07**
or
Explain series RLC circuit in detail.
- Q.4** (a) What is mesh analysis? Explain in detail with suitable example **07**
(b) Explain the time domain behavior of two port passive network. **07**
- Q.5 Write a short note (any two) 14**
(a) Hybrid parameter
(b) Superposition theorem
(c) Maximum power transfer theorem

.....