

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-I &II (SPFU) EXAMINATION – SUMMER-2019****Subject Code: ENG005****Date: 06/06/2019****Subject Name: Liner Electrical Networks****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain pole-zero construction of RLC series circuit. **07**
(b) Explain maximum power transfer theorem. Also discuss its advantages and disadvantages. **07**
- Q.2** (a) What is Laplace transform? Explain importance and applications of Laplace transform. **07**
(b) Find Laplace transform of $f_1(t) = \cos \omega t$ and $f_2(t) = e^{-at} \sin \omega t$. **07**
- Q.3** (a) Explain Thevenin's theorem. **07**
(b) Explain z-parameter in terms of h-parameter. **07**
- Q.4** (a) What is meant by poles and zeros of a network function? What is the significance of poles and zeros? Discuss the restrictions on locations of poles and zeros of transfer functions. **07**
(b) Explain the Superposition Theorem. **07**
- Q.5** (a) Explain Initial Conditions in Circuit which Contain Resistor and Inductor. **07**
(b) Explain necessary conditions for Transfer Function. **07**
- Q.6** (a) Explain Duality. **07**
(b) Derive equation of resonant frequency for parallel resonance condition. Compare series resonance with parallel resonance. **07**
- Q.7** (a) Explain Series resonance condition with concept of Q-factor. **07**
(b) State and Prove Convolution Integral. **07**
