

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**BE - SEMESTER-IV (NEW) EXAMINATION – SUMMER 2021**

Subject Code:2140305

Date:06/09/2021

Subject Name:Analog Circuits-II

Time:02:30 PM TO 05:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
<b>Q.1</b>	(a) What is capacitive and inductive crosstalk?	<b>03</b>
	(b) Draw and explain the circuit diagram of the DC Amplifier.	<b>04</b>
	(c) Why do we use the instrumentation amplifier? What is difference between differential and instrumentation amplifier? Draw the circuit diagram of Instrumentation amplifier and mention the gain equation.	<b>07</b>
<b>Q.2</b>	(a) What are the safety standards required for the medical amplifier?	<b>03</b>
	(b) Explain the mechanism of cooling and mention the advantages of a heat sink.	<b>04</b>
	(c) Write a note on grounding and shielding techniques.	<b>07</b>
<b>OR</b>		
	(c) What is the role of Isolation amplifier? Mention the types of isolation amplifier. Explain any one isolation amplifier in detail.	<b>07</b>
<b>Q.3</b>	(a) What are the problems associated with power supplies?	<b>03</b>
	(b) Differentiate between linear power supplies and switching power supplies.	<b>04</b>
	(c) Draw and explain the block diagram of a linear power supply.	<b>07</b>
<b>OR</b>		
<b>Q.3</b>	(a) Define the following parameters in detail. 1) Noise Floor 2) SNR 3) Noise corner frequency	<b>03</b>
	(b) Write a note on Shot Noise. Also, mention the equation for the shot noise calculation.	<b>04</b>
	(c) Write a brief note on noise colors.	<b>07</b>
<b>Q.4</b>	(a) Define the below-given terms. 1) Active vs Passive Filter 2) Analog vs Digital filter	<b>03</b>
	(b) Design 2 <sup>nd</sup> order low pass filter circuit for cut of frequency 1.5 kHz.	<b>04</b>
	(c) Draw and explain 1 <sup>st</sup> order wide bandpass filter for cut off frequency 500 Hz and 1500 Hz.	<b>07</b>
<b>OR</b>		
<b>Q.4</b>	(a) What is need for modulation?	<b>03</b>
	(b) Draw a circuit diagram of notch filter for the cut off frequency 50 Hz.	<b>04</b>
	(c) Write a note on amplitude modulation generation techniques.	<b>07</b>
<b>Q.5</b>	(a) Explain the need for pulse modulation.	<b>03</b>
	(b) What is the amplitude modulation? Derive the mathematical expression for amplitude modulation.	<b>04</b>
	(c) Comparison between PAM, PWM, and PPM.	<b>07</b>

**OR**

- Q.5** (a) Draw and explain the block diagram of FM Transmitters. **03**  
(b) What is frequency modulation? Derive the mathematical expression for frequency modulation. **04**  
(c) Explain the working principles of CRO with the help of a block diagram. **07**

\*\*\*\*\*