

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-IV (NEW) EXAMINATION – SUMMER 2021****Subject Code: 2141002****Date:03/09/2021****Subject Name: Analog Circuit Design****Time:02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

- Q.1** (a) Define the following parameters of Op-Amp: **03**  
1) Slew Rate  
2) CMRR  
3) UGB
- (b) Draw and explain block diagram of Op-amp. **04**
- (c) What is RC Phase shift oscillator? Brief and derive with necessary equations. **07**
- Q.2** (a) Explain transfer characteristics of an ideal Op-amp? **03**
- (b) What is an oscillator? Explain the concept of oscillation with Barkhausen criteria. **04**
- (c) Draw the hybrid  $\Pi$  model for a single stage CE transistor amplifier having load resistance  $R_L$  and obtain the expression for short circuit current gain. **07**
- OR**
- (c) Draw the hybrid  $\Pi$  model for a transistor in CE configuration and derive the expression for trans conductance  $g_m$ . Justify the validity of this model. **07**
- Q.3** (a) Define the following terms **03**  
1) Input offset voltage  
2) Thermal Drift  
3) Total output offset voltage
- (b) Discuss How op-amp can be used as current to voltage converter. **04**
- (c) Derive expression for closed loop gain of a voltage series feedback amplifier using op-amp. **07**
- OR**
- Q.3** (a) Explain the precision rectifier and draw half wave precision rectifier circuit. **03**
- (b) Discuss the features of LM317 Regulator. **04**
- (c) Show how Op-Amp can be used as summing, scaling and averaging amplifiers using non inverting configuration. **07**
- Q.4** (a) Draw clipper and clamper circuit with waveform using op-amp **03**
- (b) Draw and explain peak detector. **04**
- (c) An astable 555 Oscillator is constructed using the following components, **07**  
 $R_1 = 1k\Omega$ ,  $R_2 = 2k\Omega$  and capacitor  $C = 10\mu F$ . Calculate the output

frequency from the 555 oscillator and the duty cycle of the output waveform.

**OR**

- Q.4** (a) What is SMPS ? Discuss it's advantages and disadvantages. **03**  
(b) Explain zero crossing detector with circuit diagram and waveform. **04**  
(c) Draw and explain Op-amp based two-sided voltage limiter circuit and its response. **07**
- Q.5** (a) Differentiate between active and passive filters. **03**  
(b) Discuss magnitude and frequency scaling in filter design. **04**  
(c) Draw sallen-key LPF and derive its transfer function. **07**

**OR**

- Q.5** (a) State the properties of Butterworth filter. **03**  
(b) Draw the block diagram of PLL and explain each block. **04**  
(c) Show how Bi-quad circuit can be used as a universal filter? **07**

\*\*\*\*\*