

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VII (NEW) EXAMINATION – SUMMER 2021****Subject Code:2170906****Date:03/08/2021****Subject Name:Advanced Power Electronics****Time:10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks

- Q.1**
- (a) What is the need of multi-level inverter? Give its classifications. **03**
- (b) What do mean by switch mode power supply? How is it differs from linear regulated power supply? **04**
- (c) Draw necessary waveforms and explain working of Boost converter in continuous and discontinuous conduction mode. **07**
- Q.2**
- (a) What do you mean by hard and soft switching? How does the ZCS and ZVS principle help to achieve soft switching? **03**
- (b) Explain half bridge dc-dc converter with neat diagram and waveforms. **04**
- (c) Explain three level diode clamped type multi-level inverter. What are demerits of this topology? **07**
- OR**
- (c) Discuss operation of a five level flying capacitor multilevel inverter with neat circuit diagram and waveforms. **07**
- Q.3**
- (a) List the possible combinations or configurations of the phase shifting transformers for the 18-pulse converter clearly indicating the phase shift from the respective windings/transformer. **03**
- (b) Calculate the total no. of switches and power supply required in case of nine level cascade H-bridge inverter connected to a single phase load? Also calculate the minimum number of switches required in case of DC power supply with unequal magnitudes. **04**
- (c) Which harmonics are dominant in line for a 12-pulse multi-pulse converter? Also, explain how harmonic cancellation occurs in multi-pulse converter. **07**
- OR**
- Q.3**
- (a) Explain the role of transformer in isolated DC-DC converter. **03**
- (b) Draw circuit diagram and waveforms of output voltage and input line current in case of six-pulse diode rectifier connected to resistive load. **04**
- (c) Discuss operation of Cuk converter. Derive the relation between duty ratio and input voltage. **07**
- Q.4**
- (a) Explain the significance of third winding in case of forward converter. **03**
- (b) Classify carrier-based PWM technique for multilevel inverter. Discuss any one in detail. **04**
- (c) Discuss operation of parallel load resonant DC to DC converter. **07**
- OR**
- Q.4**
- (a) Draw block diagram of HVDC transmission system. Mention equipment required for HVDC system. **03**
- (b) Give comparison of SVC and STATCOM. **04**

- (c) With neat circuit diagram and waveform discuss class E resonant inverter. **07**
- Q.5** (a) Define FACTS. Give classification of FACTS controllers. **03**
(b) Give comparison of HVAC and HVDC transmission. **04**
(c) Explain working of STATCOM with neat diagram. **07**
- OR**
- Q.5** (a) Discuss importance of reactive power compensation. **03**
(b) Write the advantages and limitations of SSSC. **04**
(c) Explain working of FC-TCR with neat diagram and waveforms. **07**
