

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III (NEW) EXAMINATION – SUMMER 2021****Subject Code:3131704****Date:06/09/2021****Subject Name:Digital Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) 1. Give logic diagram and truth-table of EX-OR Gate 2. Subtract $(3250-72532)_{10}$ using 10s compliment 3. $F = x y + x' y' + y' z$ implement with gates	03
	(b) Define : 1) Fan in 2) Fan out 3) Propagation Delay 4) Noise margin	04
	(c) Design the full adder and full subtractor	07
Q.2	(a) Covert to another canonical form 1. $F(A,B,C) = \sum(1,7)$ 2. $F(W,X,Y,Z) = \prod(1,2,5,15)$ 3. $F(a,b,c,d,e) = \sum(1,2,7,8,9,10,11,13,14,23)$	03
	(b) State and prove De Morgan's Law. Find the complement of $F(A,B,C) = \sum(1,7)$	04
	(c) Design 3 – bit Gray code to binary code converter.	07
OR		
(c)	Draw the logic diagram of 3:8 Decoder and write the truth table. Explain its operation.	07
Q.3	(a) Simplify: $A'B + A'BC' + A'BCD + A'BC'D'E$	03
	(b) Implement the following Boolean function $F = (A + B')(CD + E)$ with NAND gates	04
	(c) List the characteristics of Logic families. Explain DTL logic family in brief	07
OR		
Q.3	(a) Explain combinational logic circuit and sequential logic circuit	03
	(b) Reduce using K-mapping the expression $F = \sum(1,5,6,12,13,14) + d(2,4)$ where d is don't care condition. Find out SOP	04
	(c) Simplify the Boolean function using the tabulation method $F(A,B,C,D,E,F,G) = \sum(20,28,38,39,52,60,102,103,127)$	07
Q.4	(a) Explain the operation of master slave J-K flip flop	03
	(b) Write the note on SR and JK Flip Flop	04
	(c) Simplify the following Boolean function $F(A,B,C,D) = \sum(0,1,2,5,8,9,10)$. Implement the simplified equation using NAND gates only	07
OR		
Q.4	(a) Explain the working of 3-bit Ring counter with necessary diagram using negative edge triggered D flip - flop.	03
	(b) Design a combinational circuit that will detect identical bits for 2 bit number	04
	(c) Explain BCD Ripple counter and draw its logic diagram and timing diagram	07

- Q.5** (a) Write a note on ALU **03**
 (b) Explain arithmetic, logic and shift micro operation **04**
 (c) Design a counter using D-flip flop, having the state diagram as **07**



OR

- Q.5** (a) Realize Ex-OR gate and NOT gate using NOR gate. **03**
 (b) Explain state table, state diagram with example. **04**
 (c) Explain 4 bit magnitude comparator with necessary Boolean expression. **07**
