

GUJARAT TECHNOLOGICAL UNIVERSITY
BE - SEMESTER-IV (NEW) EXAMINATION – SUMMER 2022

Subject Code:2141002**Date:23-06-2022****Subject Name:Analog Circuit Design****Time:10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

	MARKS
Q.1 (a) List characteristics of an ideal Op-amp.	03
(b) Define the following parameters of Op-Amp:	04
(i) Slew Rate	
(ii) CMRR	
(iii) Input offset voltage	
(iv) Input bias current	
(c) Draw the hybrid II common emitter transistor model. Derive the expression for input conductance.	07
 Q.2 (a) Draw and explain block diagram of Op-amp.	03
(b) List the parameter those affecting to the transistor at high frequencies.	04
(c) Derive the expression for the frequency for the RC phase shift oscillator using transistor.	07
OR	
(c) Write a short-note on crystal oscillator.	07
 Q.3 (a) For Hybrid- π transistor model $g_m = 50 \text{ mA/V}$, $r_{b'e} = 1 \text{ K}$, $C_e = 1 \text{ pF}$, and $C_c = 0.2 \text{ pF}$ is given then determine the values of f_β and f_T .	03
(b) Explain in detail working of Inverting amplifier in open loop op-amp configuration.	04
(c) Derive expression for closed loop gain of a voltage series feedback amplifier using op-amp.	07
OR	
Q.3 (a) Define the following parameters of Op-Amp:	03
(i) PSRR	
(ii) Unity Gain Bandwidth	
(iii) Thermal Drift	
(b) Draw and explain the op amp as an averaging amplifier.	04
(c) Explain the ideal integrator. What are the problems associated with this configuration? How it can overcome?	07
 Q.4 (a) What is the difference between active and passive filters?	03
(b) Explain Op-amp based Zero Crossing Detector with circuit diagram and waveforms.	04
(c) What is instrumentation amplifier? With help of neat diagram explain operation of Three OP-AMP based Instrumentation amplifier.	07
OR	
Q.4 (a) Draw simplified internal block diagram of 555 Timer IC.	03
(b) Explain the magnitude characteristic of band pass and band stop filter.	04

- (c) Write a short note on first order low-pass butterworth filter. **07**
- Q.5** (a) Draw and explain schematic symbol for the op-amp. **03**
(b) List advantages of Schmitt trigger over the conventional comparators. **04**
(c) Explain with the circuit diagram and waveforms, the monostable multivibrator using 555 timer. **07**

OR

- Q.5** (a) What do you mean by Voltage regulator? List different types of voltage regulators. **03**
(b) Draw and explain triangular wave generator circuit using Op-amp. **04**
(c) What is PLL? Explain operation of PLL with basic blocks and mention any four applications of it in radio communication. **07**
