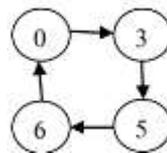


GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER– III (NEW) EXAMINATION – SUMMER 2022****Subject Code:3131704****Date:11-07-2022****Subject Name:Digital Electronics****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) What do you mean by universal gates? Implement NOT, AND, OR with any one universal gate.	03
	(b) Explain De Morgan's theorem and associative law with suitable example.	04
	(c) Design 3 – bit Gray code to binary code converter.	07
Q.2	(a) Define the following: 1) Noise Margin 2) Propagation Delay 3) Fan IN-Fan OUT	03
	(b) Expand $A+BC'+ABD'+ABCD$ to min terms and max terms.	04
	(c) Reduce using mapping the expression $\Sigma m(0,1,2,3,5,7,8,9,10,12,13)$ using K-map and implement it with NAND gate.	07
OR		
(c)	Minimize and implement the following output functions using K-map $F1=\Sigma m(1,2,3,6,8,12,14,15)$ $F2=\Pi M(3,4,5,7,11,13,15)+D(6,8)$	07
Q.3	(a) Reduce the expression $(B+BC)(B+B'C)(B+D)=B$	03
	(b) With neat sketch explain the operation of clocked RS flip flop with NAND and NOR gates.	04
	(c) Design two bit magnitude comparator with necessary diagram and equations.	07
OR		
Q.3	(a) Explain transistor transistor logic for NAND gate.	03
	(b) Explain half and full adder with necessary diagram and truth table.	04
	(c) Explain master and slave flip flop with necessary diagram.	07
Q.4	(a) How does an encoder differ from a decoder?	03
	(b) Explain BUS transfer logic for two registers.	04
	(c) Design a type T counter for given state diagram.	07

**OR**

Q.4	(a) Differentiate between sequential logic and combinatorial logic.	03
	(b) Explain arithmetic and logic micro operation.	04
	(c) Explain 2 bit up counter using JK flip flop with K-map equations and circuit diagram.	07
Q.5	(a) Explain 4 *1 multiplexer with diagram and truth table.	03
	(b) Derive JK and D flip-flop excitation tables from their truth tables.	04

- (c) Minimize the following function using tabulation method: **07**
 $F(w, x, y, z) = \sum (0,1,2,8,10,11,14,15)$

OR

- Q.5** (a) Write a note on ALU. **03**
(b) Explain BCD adder with diagram and truth table. **04**
(c) List out different types of memories used in digital logic circuits and define them. **07**
