

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER– III (NEW) EXAMINATION – SUMMER 2022****Subject Code:3132003****Date:15-07-2022****Subject Name:Design Concepts in Basic Electronics****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

- Q.1** (a) Write short note on intrinsic and extrinsic semiconductor materials. **03**
 (b) Give detail comparison of analog and digital systems. **04**
 (c) Explain digital system with block diagram and its functional elements. Also explain different functions of digital system. **07**
- Q.2** (a) Design and explain half adder combinational logic circuit. **03**
 (b) Briefly explain min-terms and max-terms with suitable example. **04**
 (c) Reduce the given Boolean Expression to its simplest possible form, compare the truth tables and implement them using minimum number of logic gates. **07**

$$\mathbf{A[B + A'B(B + A'C)']}$$

OR
 (c) Simplify the following function using K-Map method. Also implement the circuit for minimized function using logic gates. **07**

$$F(A, B, C, D) = \Pi\{0,1,2,4,5,6,8,10,12,13,15\}$$
- Q.3** (a) What is the effect of temperature on barrier potential? Explain in detail. **03**
 (b) Explain forward bias V-I characteristics of PN junction diode. **04**
 (c) Explain significance of voltage Doubler, Tripler and Quadrupler circuits. **07**
OR
- Q.3** (a) Prove $(A + B)(A + C) = A + BC$ using Boolean Algebra. **03**
 (b) Explain reverse bias V-I characteristics of PN junction diode. **04**
 (c) Explain different types of gates with their symbols and truth tables used in digital system. **07**
- Q.4** (a) Design 1-Bit magnitude comparator. **03**
 (b) Explain Capacitor Filter for bridge rectifier with circuit diagram and waveforms. **04**
 (c) Explain input and output characteristics of CB configuration of transistor. **07**
OR
- Q.4** (a) What are the applications of Transistor-Transistor Logic (TTL) circuits? **03**
 (b) Write a short note on D Flip-Flop. **04**
 (c) Attempt the following questions: **07**
 1. Perform binary multiplication of $(101)_2$ and $(111)_2$.
 2. Convert $(11011)_2$ to Grey code.
 3. Express $(-39)_{10}$ as 8-bit binary number using sign bit method.
 4. Convert $(F37A)_{16}$ to binary number.
 5. Convert $(2469)_{10}$ to BCD using 8421 code.
 6. Convert $(1011)_2$ to decimal number.
 7. Convert $(237)_8$ to decimal number.

- Q.5** (a) Explain 3-bit decoder. **03**
(b) Explain series clipper circuit with circuit diagrams and waveforms. **04**
(c) Explain positive, negative and biased clamper circuits with circuit diagrams and waveforms. **07**

OR

- Q.5** (a) Explain SERIAL IN/PARALLEL OUT shift register. **03**
(b) Explain parallel clipper circuit with circuit diagram and waveforms. **04**
(c) Explain 3-bit Asynchronous Counter in detail. **07**
