

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE – SEMESTER- VII EXAMINATION-SUMMER 2023****Subject Code: 3172413****Date: 28/06/2023****Subject Name: Advanced Power Electronics Devices and Interface Circuits****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		<b>MARKS</b>
<b>Q.1</b>	(a) Explain the concept of WBG Power Semiconductor Devices.	<b>03</b>
	(b) State the advantages and applications of WBG devices.	<b>04</b>
	(c) Compare SiC devices with Si devices.	<b>07</b>
<b>Q.2</b>	(a) Discuss role of driver circuit in Power electronics.	<b>03</b>
	(b) Draw the pin diagram of IR2110 and explain briefly its pins.	<b>04</b>
	(c) Explain requirement & importance of Isolation in power electronics.	<b>07</b>
	<b>OR</b>	
	(c) Draw the schematic of relay driver ULN 2803 for driving a motor load using a microcontroller. Explain its working.	<b>07</b>
<b>Q.3</b>	(a) Enlist isolated and non-isolated driver ICs.	<b>03</b>
	(b) Write short note on Current Transformer.	<b>04</b>
	(c) Explain Hall effect current sensors in detail.	<b>07</b>
	<b>OR</b>	
<b>Q.3</b>	(a) Draw pin diagram of single switch driver IC (e.g. TLP250).	<b>03</b>
	(b) Explain the Galvanic Isolation & its importance.	<b>04</b>
	(c) Discuss Voltage Measurement using LEM LV 25-P.	<b>07</b>
<b>Q.4</b>	(a) Draw schematic diagram of isolated linear amplifier.	<b>03</b>
	(b) Explain in brief voltage measurement using Op-amp.	<b>04</b>
	(c) Discuss F to V Converter.	<b>07</b>
	<b>OR</b>	
<b>Q.4</b>	(a) Explain the Power Scope.	<b>03</b>
	(b) State applications of Logic Analyzer.	<b>04</b>
	(c) Discuss high frequency design of Inductor for DC-DC converter circuit with appropriate example.	<b>07</b>
<b>Q.5</b>	(a) Which type of core is required for high frequency switching applications? State different types of cores used in practice.	<b>03</b>
	(b) Explain Transformer Design for Forward converter.	<b>04</b>
	(c) Explain the Natural Cooling & forced Cooling of Heat Sinks.	<b>07</b>
	<b>OR</b>	
<b>Q.5</b>	(a) What is energy equation of inductor?	<b>03</b>
	(b) Compare active and passive heat sink.	<b>04</b>
	(c) Give the concept of thermal resistance. Describe the analogy between thermal and Electrical quantities.	<b>07</b>

\*\*\*\*\*