

Enrolment No./Seat No_____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-IV (NEW) EXAMINATION – SUMMER 2024

Subject Code:2141002

Date:15-07-2024

Subject Name:Analog Circuit Design

Time:10:30 AM TO 01:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

- Q.1** (a) Draw and explain block diagram of an op-amp. **03**
(b) Draw Hybrid- π equivalent circuit for CE transistor. Also derive the equation of transconductance g_m . **04**
(c) What is an oscillator? Explain the concept of oscillation with Barkhausen criteria. **07**
- Q.2** (a) Define following terms : **03**
(1) CMRR
(2) Input Bias Current
(3) Input Offset Current
(b) Explain the characteristics of ideal op-amp. **04**
(c) Draw and explain with necessary figure the single stage CE amplifier response. Also explain the significance of Gain Bandwidth product. **07**
- OR**
- (c) Explain application of an op-amp as summing, scaling and averaging amplifier (Inverting configuration). **07**
- Q.3** (a) Draw and explain voltage transfer characteristics of an op-amp. **03**
(b) Draw BJT based emitter coupled differential amplifier circuit. How can we improve its CMRR? **04**
(c) Draw and explain op-amp based wien-bridge oscillator circuit and obtain frequency of oscillator. **07**
- OR**
- Q.3** (a) What is thermal drift? How does it affect the performance of an op-amp circuit? **03**
(b) Explain Voltage to Current convertor using op-amp with ground load. **04**
(c) Draw and explain voltage shunt feedback amplifier, also derive expression for Input resistance, Output resistance. **07**
- Q.4** (a) Define slew rate of an op-amp. What are its causes? **03**
(b) Explain operation of PLL with basic block diagram. **04**
(c) Explain the basic differentiator using an op-amp. Obtain expression for output voltage with necessary waveforms. **07**
- OR**
- Q.4** (a) What do you understand by precision rectifier? Draw half wave precision rectifier circuit. **03**
(b) Draw and explain Schmitt trigger circuit. **04**
(c) Explain with a neat diagram and waveforms, the operation of a monostable multivibrator using 555 timer. **07**
- Q.5** (a) Explain zero crossing detector with circuit diagram and wave forms. **03**
(b) Discuss magnitude scaling and frequency scaling in filter design. **04**
(c) Show how Bi-quad circuit can be used as a universal filter. **07**

OR

- Q.5** (a) Compare active and passive filter. **03**
(b) Compare linear and switching mode regulators. **04**
(c) Draw Sallen and Key low pass filter circuit and obtain its transfer function. **07**
