

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III (NEW) EXAMINATION – SUMMER 2024****Subject Code:3131704****Date:16-07-2024****Subject Name: Digital Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

MARKS

- | | | |
|------------|--|-----------|
| Q.1 | (a) Briefly explain any three types of number systems with suitable example. | 03 |
| | (b) Convert 1) (0.513) decimal to octal and 2) (630.4) octal to decimal. | 04 |
| | (c) Explain all different types of Digital Logic Gates with proper truth tables and diagrams. | 07 |
| Q.2 | (a) What is Boolean algebra? Explain in brief its various laws. | 03 |
| | (b) Explain binary addition and binary subtraction with suitable example. | 04 |
| | (c) What is combinational circuit? Explain half adder circuit with proper truth table, equations and circuit diagram. | 07 |
| | OR | |
| | (c) With proper truth table, equations and truth table explain full adder circuit. Also justify that full adder can be implemented using two half adders. | 07 |
| Q.3 | (a) Briefly explain the concept of multiplexer (MUX). | 03 |
| | (b) What is Sum of Product form of Boolean equation? Explain with example. | 04 |
| | (c) Implement the following function with NAND gates
$F(x,y,z) = \sum(0,6)$ | 07 |
| | OR | |
| Q.3 | (a) Briefly explain the concept of Demultiplexer (De MUX). | 03 |
| | (b) What is Product of Sum form of Boolean equation? Explain with example. | 04 |
| | (c) Implement the following function with NOR gates
$F(x,y,z) = \sum(0,6)$ | 07 |
| Q.4 | (a) What is sequential circuit? Briefly explain it. | 03 |
| | (b) Briefly explain decoder. | 04 |
| | (c) With suitable diagram and truth table explain D Flip Flop. | 07 |
| | OR | |
| Q.4 | (a) What is register? Briefly explain it. | 03 |
| | (b) Briefly explain encoder. | 04 |
| | (c) With suitable diagram and truth table explain J-K Flip Flop. | 07 |
| Q.5 | (a) Explain the following terms. 1) Fan in 2) Fan out 3) Propagation Delay | 03 |
| | (b) With suitable diagram explain shift register. | 04 |
| | (c) Explain various types of memories in detail. | 07 |
| | OR | |
| Q.5 | (a) Explain the terms.1) Threshold Voltage 2) Noise Margin 3) Power dissipation | 03 |
| | (b) With suitable diagram explain synchronous counter. | 04 |
| | (c) With suitable diagram explain 3 states TTL gate. | 07 |
