

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-III (NEW) EXAMINATION – SUMMER 2024****Subject Code:3132003****Date:29-06-2024****Subject Name: Design Concepts in Basic Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
<b>Q.1</b>	(a) Explain the significance of the binary number system in digital electronics.	<b>03</b>
	(b) Differentiate between analog system and digital system.	<b>04</b>
	(c) Explain Excess-3 code and gray code.	<b>07</b>
<b>Q.2</b>	(a) Simplify the Boolean expression $F=A'B+AB'+AB$ using Boolean algebraic laws. Show each step of the simplification process.	<b>03</b>
	(b) Describe the purpose of parity bits in error detection and correction, and illustrate with an example how parity bits are used to detect errors in data transmission.	<b>04</b>
	(c) Describe the operation of a multiplexer (MUX) and its application in digital circuits. Provide a schematic diagram of a 4-to-1 MUX and explain how it selects one of four input data lines based on the control inputs.	<b>07</b>
<b>OR</b>		
	(c) Discuss the application of Gray code in rotary encoders. Explain how Gray code prevents errors during rotational movement sensing and provide a real-world example to support your explanation.	<b>07</b>
<b>Q.3</b>	(a) Explain the operation of a half-adder circuit and draw its logic diagram using basic logic gates. Include the truth table for the half-adder.	<b>03</b>
	(b) Explain role of multiplexer in digital electronics, explain with diagram.	<b>04</b>
	(c) Draw truth table and logic diagram of 3 to 8 line decoder.	<b>07</b>
<b>OR</b>		
<b>Q.3</b>	(a) What are POS forms of Boolean Expression?	<b>03</b>
	(b) Differentiate between a latch and a flip-flop, highlighting their differences in functionality and application.	<b>04</b>
	(c) Design a 4-bit binary adder circuit using full-adder modules. Explain the operation of the circuit and provide the truth table for the 4-bit addition.	<b>07</b>
<b>Q.4</b>	(a) State application of counters.	<b>03</b>
	(b) Classify the various modes of operation of shift registers.	<b>04</b>
	(c) Draw the logic diagram of a 4-bit parallel-in-parallel-out (PIPO) register using D flip-flops. Explain how data is loaded into and read from the register	<b>07</b>
<b>OR</b>		
<b>Q.4</b>	(a) Explain the difference between conductors, semiconductors, and insulators based on their electrical conductivity. Provide examples of materials belonging to each category and discuss their applications?	<b>03</b>
	(b) Explain the term "fan-in" in the context of logic families. Describe how fan-in affects the performance and reliability of digital circuits.	<b>04</b>
	(c) Explain the voltage Doubler, Tripler and Quadrupler circuits in details.	<b>07</b>

- Q.5** (a) Calculate the average output voltage of a half-wave rectifier circuit with a sinusoidal input voltage. Consider the ideal diode model and neglect any ripple voltage. **03**
- (b) Explain the load line analysis for diode. **04**
- (c) Draw the output waveform of a full-wave rectifier circuit with a sinusoidal input voltage. Label the key points such as peak voltage, average voltage, and ripple voltage. **07**

**OR**

- Q.5** (a) Draw the circuit diagram of a common-emitter transistor amplifier with base biasing. Explain the purpose of the biasing resistors and how they set the operating point of the transistor. **03**
- (b) Explain biased negative clamper circuit. **04**
- (c) Compare and contrast the base and collector characteristic curves of a BJT with different values of  $\beta$  (current gain). Discuss how variations in  $\beta$  affect the shape and slope of the curves. **07**

\*\*\*\*\*