

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III (NEW) EXAMINATION – SUMMER 2024

Subject Code:3134104

Date:06-07-2024

Subject Name: Electronic Devices and Circuits

Time:10:30 AM TO 01:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) Explain the formation of depletion region when p-type and n-type materials are combined.	03
	(b) Explain effect of temperature on various parameters of a transistor.	04
	(c) Draw and Explain Full wave bridge rectifier circuit.	07
Q.2	(a) Draw and explain V-I (voltage- current) characteristics of Zener diode.	03
	(b) What is DC load line? Explain with necessary diagram how it can be applied to find operating point in a given circuit.	04
	(c) Explain construction and working of N-channel MOSFET.	07
OR		
(c)	Explain Darlington pair connections of two transistors.	07
Q.3	(a) Describe JFET applications as constant current source.	03
	(b) Compare CE, CB and CC configurations of a transistor and their applications.	04
	(c) Justify the need of transistor biasing. Explain voltage divider bias of common emitter amplifier in brief.	07
OR		
Q.3	(a) Explain how transistor can be operated as a switch.	03
	(b) Draw and explain series negative clipper waveform with input and output waveforms.	04
	(c) Write a short note on Varactor diode.	07
Q.4	(a) Explain Principal of operation of Photodiode.	03
	(b) Derive and explain the relation between current gain α and β in a transistor.	04
	(c) Explain capacitive filter with Ripple Factor.	07
OR		
Q.4	(a) What is the application of positive feedback circuit?	03
	(b) Briefly explain about cooling system for turbo alternators.	04
	(c) Explain construction, operation and characteristic of P-channel Enhancement type MOSFET in detail.	07
Q.5	(a) Briefly explain turbine classification.	03
	(b) Compare FET with BJT.	04
	(c) Draw and explain class B push-pull amplifier.	07
OR		
Q.5	(a) Explain basic principle of a solar cell.	03
	(b) Draw Ebers-Moll model and π -model of a transistor.	04
	(c) Explain the working of a transformer coupled class A power amplifier and show the efficiency of class A transformer coupled amplifier is 50%.	07
