

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III EXAMINATION – SUMMER 2025

Subject Code:3130306

Date:06-06-2025

Subject Name:Fundamentals of Digital Electronics

Time:02:30 PM TO 05:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

- Q.1*** (a) Differentiate Analog and Digital system. **03**
(b) Covert Hexadecimal number (1A.B) to Decimal, Binary and Octal. **04**
(c) Reduce expression $F = \sum m(1, 2, 3, 4, 5, 10, 15) + d(6, 7, 12)$ using K-map and implement it using basic logic gates. **07**
- Q.2** (a) Explain Error detection codes. **03**
(b) Realize AND and OR gate using TTL. **04**
(c) Simplify to minimal expression and implement using NAND gates: $F = W + XY[(X'Z)' + (W + Z')'Y]$ **07**
- OR**
- (c) State and Prove De Morgan's Theorem. **07**
- Q.3** (a) Explain Half adder with its implementation. **03**
(b) Design full subtractor using logic gates. **04**
(c) What is Code convertor? Design 4-bit binary to gray code convertor. **07**
- OR**
- Q.3** (a) What is Encoder? Explain 4 to 2 Encoder. **03**
(b) Design 2-bit Magnitude comparator. **04**
(c) Explain Look ahead carry adder with its implementation. **07**
- Q.4** (a) What is Demultiplexer? Explain 1 to 4 Demultiplexer. **03**
(b) Differentiate PAL, PLA and PROM. **04**
(c) Explain Mealy model of sequential circuits. **07**
- OR**
- Q.4** (a) Explain functioning of RS-Flipflop. **03**
(b) Give the difference between Combinational circuits and Sequential circuits. **04**
(c) Implement function $F = \bar{A}B\bar{C} + A\bar{B}C$ using PAL. **07**
- Q.5** (a) What is Race around condition in flip-flop? How can we avoid it? **03**
(b) Describe functioning of Ring counter. **04**
(c) Explain functioning of Master-slave JK-flip flop. **07**
- OR**
- Q.5** (a) Give the applications of Flip-flops. **03**
(b) Explain working 4-bit serial-in to parallel-out shift register. **04**
(c) Implement 4-bit Asynchronous counter. **07**
