

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III EXAMINATION – SUMMER 2025****Subject Code:3131704****Date:13-06-2025****Subject Name:Digital Electronics****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) Differentiate between Combinational and Sequential circuits with suitable example.	03
	(b) Convert	04
	a. $(110101)_2$ to decimal	
	b. $(247.36)_8$ to hex number	
	(c) Explain basic laws of Boolean Algebra with appropriate illustrations.	07
Q.2	(a) Map the following SOP expression on a Karnaugh Map : $A'B'C+A'BC'+ABC'+ABC$	03
	(b) State De' Morgan's Theorem and prove it using truth table.	04
	(c) Minimize the following Boolean functions using the K map method. $F(A,B,C,D) = \sum (0,1,2,3,5,7, 8,9,11,14)$ $F(A,B,C,D) = \sum (0,1,2,5,8,9,10)$	07
OR		
	(c) Design a half adder and half subtractor circuit.	07
Q.3	(a) Minimize the four variable logic function $F(A,B,C,D)=ABC'D+A'BCD+A'B'C'+A'B'D'+AC'+AB'C+B'$	03
	(b) With the help suitable block diagram and truth table, explain n bit digital comparator.	04
	(c) Design and explain BCD to excess 3 code converter.	07
OR		
Q.3	(a) Represent the decimal number 4096 in BCD, Excess- 3 code and octal code.	03
	(b) Give comparison between TTL and CMOS logic Family.	04
	(c) Draw and explain block diagram and truth table of 4:1 line multiplexer with strobe (enable) input. Realize the 4:1 line multiplexer using NAND gate.	07
Q.4	(a) Explain clocked S-R Flipflop. State its limitations.	03
	(b) Distinguish between UVEPROM and EEPROM.	04
	(c) Draw and explain two input TTL NAND gate.	07
OR		
Q.4	(a) Differentiate between RAM and ROM.	03
	(b) Define following characteristics of Digital ICs	04
	1. Noise Immunity	
	2. Propagation Delay	
	3. Power Dissipation	
	4. Fan out	

- (c) Explain 3-bit synchronous counter using J-K flip flop. **07**
- Q.5** (a) Write short note on gray code. **03**
(b) Explain J-K flip flop converted to T-type flip flop with necessary diagram and truth table. **04**
(c) Explain various types of computer system microoperations. **07**
- OR**
- Q.5** (a) Write a brief note on 'Ripple counter'. **03**
(b) Draw and explain 3 to 8 line decoder. **04**
(c) Enlist any two primary uses of shift registers. Draw and explain 4-bit bidirectional shift register. **07**
