

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III EXAMINATION – SUMMER 2025****Subject Code:3132003****Date:31-05-2025****Subject Name:Design Concepts in Basic Electronics****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
Q.1	(a) Convert the decimal number 42 to binary, octal, and hexadecimal.	03
	(b) Write the Gray Code sequence for the numbers 0 to 7 in binary.	04
	(c) Convert the binary number 11011011 to Gray Code, Excess-3, and hexadecimal.	07
Q.2	(a) State and prove De Morgan's Theorem.	03
	(b) Simplify the Boolean expression $AB+A'B$ using Boolean laws.	04
	(c) Design a 4-to-1 Multiplexer using basic gates. Explain its working with a truth table and provide its Boolean expression.	07
OR		
Q.3	(c) Explain a 3-to-8 Decoder circuit with its truth table and applications.	07
	(a) What is the difference between synchronous and asynchronous counters?	03
	(b) Explain the working of a 3-bit asynchronous (ripple) counter. Draw its circuit diagram and truth table.	04
	(c) Describe the design and operation of a Serial In/Serial Out (SISO) and Serial In/Parallel Out (SIPO) shift register. Draw circuit diagrams and timing diagrams to illustrate the differences.	07
OR		
Q.3	(a) Describe the difference between a shift register and a counter.	03
	(b) Describe the timing delay issue in asynchronous counters and explain why it occurs.	04
	(c) Explain the working of a J-K flip-flop with a circuit diagram, truth table, and timing diagram. Discuss how it handles the race condition.	07
Q.4	(a) Explain the key features of TTL (Transistor-Transistor Logic).	03
	(b) Describe the basic circuit of RTL (Resistor-Transistor Logic) and discuss its main application.	04
	(c) Discuss the performance characteristics of digital logic families.	07
OR		
Q.4	(a) Define an intrinsic semiconductor and give one example.	03
	(b) Describe how a diode behaves in forward bias and reverse bias conditions.	04
	(c) Explain the impact of doping on the energy levels of semiconductors.	07
Q.5	(a) What is a clipper circuit? Give one practical example of its use.	03
	(b) What is the purpose of a choke-input filter? Explain how it affects the output voltage ripple.	04
	(c) Compare half-wave, full-wave center-tapped, and bridge rectifiers in terms of efficiency, PIV, ripple frequency, and transformer requirements.	07

OR

- Q.5** (a) Explain the concept of a load line in a transistor circuit. **03**
(b) Describe the process of reading a transistor data sheet and list at least three important parameters. **04**
(c) Discuss the process of accurately analyzing a Voltage-Divider Bias circuit. **07**
