

GUJARAT TECHNOLOGICAL UNIVERSITY
BE SEMESTER-VIII(OLD) EXAMINATION-WINTER 2017

Subject code: 180805**Date: 10-11-2017****Subject Name: High Voltage Engineering****Time: 02:30 pm to 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Describe with a neat sketch, the working of a Van de Graff generator. What are the factors that limit the maximum voltage obtained? **07**
- (b) Define the Townsend first & second ionization co-efficient. Also derive the equation for second ionization co-efficient $I = I_0 e^{\alpha d} / (1 - \gamma (e^{\alpha d} - 1))$. **07**
- Q.2** (a) State and explain Paschen's law. How do you account for the minimum voltage for breakdown under a given pd condition? **07**
- (b) Explain the voltage multiplier circuits working with a schematic diagram. **07**
- OR**
- (b) A ten stage Cockraft-Walton circuit has all capacitors of 0.06 μ F. The secondary voltage of the supply transformer is 100 kV at a frequency of 150 Hz. If the load current is 1 mA, determine (i) voltage regulation (ii) the ripple (iii) the optimum number of stages for maximum output voltage (iv) the maximum output voltage. **07**
- Q.3** (a) Explain working of Marks Circuit. **07**
- (b) Explain liquid purification system with test cell. **07**
- OR**
- Q.3** (a) Explain partial discharge in solid dielectrics. Discuss its effects on the dielectric strength with neat sketch. **07**
- (b) Draw & Explain how a sphere gap can be used to measure the peak value of voltage. What are the parameters and factors that influence such voltage measurement? **07**
- Q.4** (a) Explain with neat diagram the principle of operation of an Electrostatics Voltmeter. Discuss its advantages and limitations for high voltage measurements. **07**
- (b) With help of neat sketch defines front time and tail time for the impulse wave. **07**
- OR**
- Q.4** (a) What is the principle of operation of a resonant transformer? How is it advantages over the Cascade connected transformer? **07**
- (b) A 12-stage impulse generator has capacitors each rated at 0.3 μ F, 150 kV. The capacitance of the test specimen is 400 pF. Determine the wave front and wave tail resistance to produce at 1.2/50 sec. impulse wave. Also determine the maximum output voltage if the charging voltage is 125 kV. **07**
- Q.5** (a) What is meant by insulation co-ordination? How are the protective devices chosen for optimal insulation level in a power system? **07**
- (b) Explain high voltage Schering bridge for measurement of capacitance and $\tan \delta$ of an insulator. **07**
- OR**
- Q.5** (a) Discuss measurement of Dielectric Constant & Loss tangent of capacitor and also derive the equation for the same. **07**
- (b) Explain High voltage Test on insulator. **07**