

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**BE- SEMESTER- 1<sup>st</sup> / 2<sup>nd</sup> • EXAMINATION – WINTER 2018**

**Subject Code:110005****Date: 18/01/2019****Subject Name: Elements of Electrical Engineering****Time:10:30 AM TO 1:00 PM****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Derive an expression for temperature coefficient at temperature  $t$ ,  $\alpha_t = \alpha_0 / (1 + \alpha_0 t)$ . Where notation have usual meaning. **07**
- (b) Derive an expression for calculating equivalent star to delta transformation. **07**
- Q.2** (a) The resistance of a certain length of wire is  $4.6 \Omega$  at  $20^\circ \text{C}$  and  $5.68 \Omega$  at  $80^\circ \text{C}$ . Determine (i) temperature co-efficient of resistance of the material of wire at  $0^\circ \text{C}$  (ii) resistance of wire at  $60^\circ \text{C}$ . **07**
- (b) Find the effective resistance of the network shown in Figure I. **07**

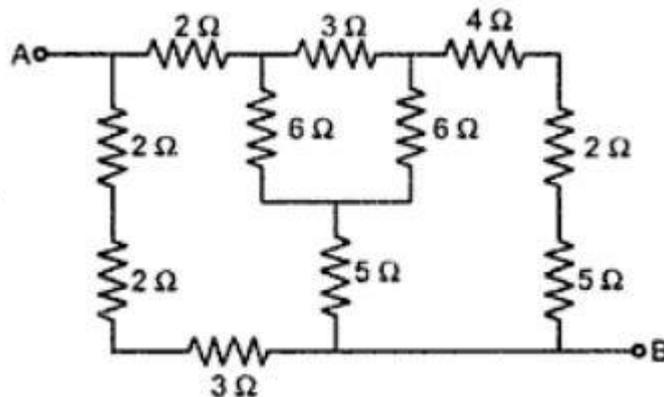


Fig. I

- Q.3** (a) Compare electric circuit with magnetic circuit. **07**
- (b) Two metal plates of area  $100 \text{ cm}^2$  are separated by a dielectric of a 2 mm having a relative permittivity of 5. When a dc voltage of 500 V is applied across the capacitor plates, find (i) capacitance (ii) charge on the capacitor (iii) electrical field strength and (iv) electric flux density. **07**
- Q.4** (a) Define capacitance. Derive an expression for the total capacitance of a group of capacitance when (i) they are connected in series (ii) they are connected in parallel. **07**
- (b) Two coils having 100 and 1000 turns respectively have common magnetic circuit of 25 cm diameter and  $625 \text{ cm}^2$  cross-section and a constant relative permeability of 2000. Calculate, **07**
- (i) Self inductance of both the coils
  - (ii) Mutual inductance between them if the co-efficient of coupling is 0.5.

- Q.5** (a) Prove that current in purely inductive circuit lags its voltage by  $90^\circ$  and average power consumption in pure inductor is zero. **07**
- (b) An air-cored choke coil takes a current of 3 A and dissipates 200 W, when connected to 200 V, 50 Hz supply. In another similar coil, current is 3 A and power is 270 W under the same conditions. Calculate the (i) current taken (ii) power factor (iii) total power absorbed when two coils are connected in series to the same supply. **07**
- Q.6** (a) State relation between line voltage and phase value of voltage and current for (i) Balanced star connected load. **07**  
(ii) Balanced delta connected load.
- (b) Explain variation of wattmeter readings for 3-phase power measurement by two watt method as power factor takes values of unity, 0.5, between 0.5 and 0 and 0. **07**
- Q.7** (a) Explain charging of battery from AC supply with schematic diagram. **07**
- (b) Explain construction of cable. Explain each part and its importance. **07**

\*\*\*\*\*