

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER- 1st / 2nd EXAMINATION (NEW SYLLABUS) – WINTER 2018

Subject Code: 2110005

Date: 18/01/2019

Subject Name: Elements of Electrical Engineering

Time: 10:30am to 01:00pm

Total Marks: 70

Instructions:

1. Question No. 1 is compulsory. Attempt any four out of remaining Six questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

Q.1	Objective Question (MCQ)	Mark
(a)		07
1.	A kilowatt hour is the unit of [a] Energy [b] power [c] electric charge [d] electric current	
2.	An ideal voltage source should have [a] zero internal resistance [b] infinite source resistance [c] large value of e.m.f. [d] low value of e.m.f.	
3.	A wave completes one cycle in 10 μ s. Its frequency will be [a] 10 μ Hz [b] 50 Hz [c] 100 KHz [d] 10 KHz	
4.	If a pure capacitance is connected to an a.c. source, the current _____ the source voltage by _____ [a]Lags, 90 ⁰ [b] lags, 45 ⁰ [c] leads,90 ⁰ [d] leads, 45 ⁰	
5.	When two capacitors of 6 μ F and 12 μ F are connected in series, their effective value will be [a] 18 μ F [b] 6 μ F [c] 4 μ F [d] μ F	
6.	An R-L circuit has a resistance of 3 ohms and a reactance of 4 ohms. The impedance of the circuit is [a]5 ohms [b] 7 ohms [c] 1 ohm [d] 25 ohms	
7.	The total lumens emitted by a source of 1 candela are equal to [a]0.4 π [b] 4 π [c] 2 π [d] 8 π	
(b)		07
1.	A network which does not have either voltage source or current source is called [a] Active network [b] Passive network [c] Resistive network [d] Dummy network	
2.	Conductivity is analogous to [a]Flux [b] reluctance [c] permeance [d] current	
3.	Tesla is the unit of [a]Flux density [b] flux [c] magnetic field strength [d] reluctance	
4.	The value of form factor is [a] 11.1 [b] 1.11 [c] 1.414 [d] 14.14	
5.	The area of hysteresis loop is a measure of [a] magnetic flux [b] permeance [c] mmf per cycle [d] energy loss per cycle	
6.	The conjugate of the complex quantity (4-j5) will be [a] -4-j5 [b] 4-j5 [c] -4+j5 [d] 4+j5	
7.	The power factor of R-C series a.c. circuit is [a] unity [b] lagging [c] leading [d] zero	

Q.2	(a) State and explain Kirchoff's voltage and current laws.	03
	(b) Define & explain temperature co-efficient of resistance.	04
	(c) Derive the equations to translate a passive electric circuits from star network to delta network configuration with diagram.	07
Q.3	(a) Derive the expression for the equivalent capacitance of capacitors connected in parallel.	03
	(b) Find out the equation for energy stored in capacitor.	04
	(c) The total capacitance of two capacitors is 0.03 F when joined in series and 0.16 F when connected in parallel. Find the capacitance of each capacitor.	07
Q.4	(a) State and explain faraday's laws of electromagnetic Induction.	03
	(b) Give similarities and dissimilarities between electrical circuit and magnetic circuit.	04
	(c) Derive the equation of coefficient of coupling of magnetically coupled coils.	07
Q.5	(a) Explain magnetic hysteresis.	03
	(b) A certain waveform has a form factor of 1.2 and a peak factor of 1.5. If the maximum value is 100, find the r.m.s. value and the average value. Prove the condition of resonance for series R-L-C a.c. circuit. Also analyze the phenomena with the help of graph.	04
	(c)	07
Q.6	(a) Explain in brief the following for 3-phase AC circuit: Phase sequence, Line voltage, Phase voltage	03
	(b) Two circuits, the impedances of which are given as $Z_1=(10+j15)$ ohms and $Z_2=(6-j8)$ ohms are connected in parallel. If the total current supplied is 15A, what is power taken by each branch? Explain in brief power measurement using two wattmeter method in 3-phase system with star connected load.	04
	(c)	07
Q.7	(a) List the different types of illumination scheme.	03
	(b) Discuss the types of cables used for residential and commercial wiring. List the different types of lamp and explain florescent lamps with wiring diagram.	04
	(c)	07
