

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III (New) EXAMINATION – WINTER 2018****Subject Code: 2130306****Date: 12/12/2018****Subject Name: Fundamentals of Digital Design****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Perform BCD addition: $456.7 + 123.4$ **03**
 (b) $(89.75)_{10} = (\text{_____})_2 = (\text{_____})_{16}$ **04**
 (c) (1) What is difference between Latch and Flip-flop? Distinguish **07**
 Combinational & Sequential circuits.
 (2) Draw truth table & symbol for NAND, NOR, EX-OR gate.
- Q.2** (a) Define Fan-in, Fan-out & Noise margin. **03**
 (b) State & Prove De-Morgan's theorem. **04**
 (c) Reduce the expression $F(A, B, C, D) = \sum m(0, 2, 6, 10, 11, 12, 13) +$ **07**
 $d(3, 4, 5, 14, 15)$ using K-map and implement the real minimal expression in universal logic.
- OR**
- (c) Reduce the expression $F(A, B, C, D) =$ **07**
 $\pi M(3, 4, 5, 7, 11, 13, 15). d(6, 8, 10, 12)$ using K-map and implement the real minimal expression in AOI logic.
- Q.3** (a) What is comparator? Design 1-bit magnitude comparator. **03**
 (b) Design 3 to 8 decoder using basic gates. **04**
 (c) What is full adder? Draw truth table & design full adder circuit. **07**
- OR**
- Q.3** (a) Design Half Subtractor using logic gates. **03**
 (b) Design 8x1 multiplexer using basic gates. **04**
 (c) Define Code converter. Design 4-bit Binary to Gray code converter. **07**
- Q.4** (a) Explain Edge triggered D- flip flop. **03**
 (b) Give the comparison between PROM, PLA & PAL. **04**
 (c) Implement the following Boolean functions using PAL with four inputs and **07**
 3-wide AND-OR structure. Also write PAL programming table.
 $F1(A, B, C, D) = \sum m(2, 12, 13)$
 $F2(A, B, C, D) = \sum m(7, 8, 9, 10, 11, 12, 13, 14, 15)$
 $F3(A, B, C, D) = \sum m(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$
- OR**
- Q.4** (a) Explain Edge triggered T- flip flop. **03**
 (b) Design a combinational circuit using a PROM. The circuit accepts a 3-bit **04**
 binary number and generates its equivalent XS-3 code.
 (c) Implement the following Boolean functions using PLA. Also write PLA **07**
 programming table.
 $F1(X, Y, Z) = \sum m(0, 1, 2, 4)$ & $F2(X, Y, Z) = \sum m(0, 5, 6, 7)$
- Q.5** (a) What is Race around condition? Give its solution. **03**
 (b) Explain operation of Edge triggered SR- flip flop with the help of truth table. **04**
 (c) Enlist the types of D to A converter & explain any one in detail. **07**

OR

- Q.5** (a) What is VHDL & ABEL? **03**
(b) Explain operation of Edge triggered JK- flip flop with the help of truth table. **04**
(c) Enlist the types of A to D converter & explain any one in detail. **07**
