

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER-III (New) EXAMINATION – WINTER 2018****Subject Code:2130902****Date:01/12/2018****Subject Name:Analog Electronics****Time:10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

|            |   | MARKS     |
|------------|---|-----------|
| <b>Q.1</b> | (a) Why is the effect of negative feedback on bandwidth?  | <b>03</b> |
|            | (b) Classify power amplifiers. Write note on Class AB push pull amplifier.  | <b>04</b> |
|            | (c) Draw and explain biasing circuits for JFET.   | <b>07</b> |
| <b>Q.2</b> | (a) Define following terms. (1) CMRR (2) PSRR (3) Slew Rate   | <b>03</b> |
|            | (b) Distinguish between Ideal and Practical OP-AMP.   | <b>04</b> |
|            | (c) Draw and explain block diagram of a typical OP-AMP.   | <b>07</b> |
| <b>OR</b>  |   |           |
|            | (c) Draw the circuit of basic integrator using OP-AMP. What are the problems associated with this configuration? How they are overcome? | <b>07</b> |
| <b>Q.3</b> | (a) Define following parameter of an OP-AMP,<br>(1) Input bias current (2) Input offset current.  | <b>03</b> |
|            | (b) How OP-AMP can be used as a difference amplifier?   | <b>04</b> |
|            | (c) Derive an expression of voltage gain for closed loop non-inverting OP-AMP.  | <b>07</b> |
| <b>OR</b>  |   |           |
| <b>Q.3</b> | (a) How OP-AMP can be used as a peak detector.?   | <b>03</b> |
|            | (b) Discuss the requirement of instrumentation amplifier along with its applications.   | <b>04</b> |
|            | (c) Draw the circuit diagram to generate triangular waveform using OP-AMP.  | <b>07</b> |
| <b>Q.4</b> | (a) Explain application of OP-AMP as a zero crossing detector.  | <b>03</b> |
|            | (b) Explain the working of RC Phase shift oscillator using OP-AMP.  | <b>04</b> |
|            | (c) Explain the working of monostable multivibrator using IC-555.   | <b>07</b> |
| <b>OR</b>  |   |           |
| <b>Q.4</b> | (a) Explain advantages and application of OP-AMP based Wien bridge oscillator.  | <b>03</b> |
|            | (b) Explain voltage to current converter circuit using OP-AMP.  | <b>04</b> |
|            | (c) Explain the operation of voltage controlled oscillator using functional block diagram.  | <b>07</b> |
| <b>Q.5</b> | (a) Write merits of active filters over passive filters.  | <b>03</b> |
|            | (b) Draw the frequency response of first order butterworth high pass filters.   | <b>04</b> |
|            | (c) Explain operation of PLL with basic blocks.   | <b>07</b> |
| <b>OR</b>  |   |           |
| <b>Q.5</b> | (a) What are the basic design consideration for designing regulated power supplies?   | <b>03</b> |
|            | (b) Draw and explain block diagram of LM-337 along with its applications.   | <b>04</b> |
|            | (c) Draw and explain circuit diagram of first order butterworth low pass filter using OP-AMP.   | <b>07</b> |

\*\*\*\*\*