

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER– III (New) EXAMINATION – WINTER 2019****Subject Code: 2130306****Date: 5/12/2019****Subject Name: Fundamentals of Digital Design****Time: 02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		MARKS
Q.1	(a) Convert number $(10.11)_2$ into decimal, hexa and octal numbers.	03
	(b) Draw the symbol and truth tables of Ex-OR, Ex-NOR, NAND and NOR logic gates.	04
	(c) Simplify the function $F = \sum(0,3,4,6,8,10,12,14)$ with and without don't care conditions $d = \sum(1,2,9,11)$ and compare results.	07
Q.2	(a) Give the full form of DL, RTL, DTL, TTL, ECL logic family.	03
	(b) Define terms: fan-in, fan-out, switching times and noise margin.	04
	(c) Simplify the following Boolean functions to a minimum numbers of literals.	07
	1. $F1 = XYZ + X'Y + XYZ'$	
	2. $F2 = (X+Y+Z)(X)(Y)(Z)$	
	3. $F3 = X + XY + XYZ + XY' + XZ'$	
	4. $F4 = A'B'C' + B'CD' + A'BCD' + AB'C'$	
OR		
	(c) Simplify the Boolean Function by using the tabulation method: $F = \sum(0,1,2,8,10,11,14,15)$	07
Q.3	(a) Explain De Morgan's Theorem and prove it.	03
	(b) Perform $(-8) - (-4)$ using 2's complement method.	04
	(c) Implement the function $F = D(A+BC) + AB'$ using NOR gates.	07
OR		
Q.3	(a) Design and explain half adder circuit.	03
	(b) Explain operation of 4:1 multiplexer with logic diagram & truth table.	04
	(c) Design a BCD adder using 4 bit parallel adder blocks and basic gates.	07
Q.4	(a) Explain types of ROMs.	03
	(b) Explain working of JK- flip-flop with diagram.	04
	(c) Design 4-bit binary to BCD code convertor.	07
OR		
Q.4	(a) Define PLA with block diagram.	03
	(b) Write a short note on shift register.	04
	(c) Design and explain 4 bit magnitude comparator.	07
Q.5	(a) Draw and explain RS flip flop.	03
	(b) Explain R-2R ladder type DAC.	04
	(c) Draw and explain 3 bit binary counter using JK flip flop.	07
OR		
Q.5	(a) Explain state diagram with example.	03
	(b) Explain successive approximation type ADC.	04
	(c) What is the full form of FPGA? Explain the basic block diagram of FPGA.	07
