

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER– III (New) EXAMINATION – WINTER 2019****Subject Code: 2130902****Date: 30/11/2019****Subject Name: Analog Electronics****Time: 02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		<b>MARKS</b>
<b>Q.1</b>	<b>(a)</b> Explain the following terms. (1) PSRR (2) Input bias current (3) Input offset Voltage	<b>03</b>
	<b>(b)</b> Draw the circuit diagram of class B push-pull amplifier & explain its working.	<b>04</b>
	<b>(c)</b> List and discuss all ideal characteristics of an Op-Amp.	<b>07</b>
<b>Q.2</b>	<b>(a)</b> What are the merits and demerits of hybrid parameters?	<b>03</b>
	<b>(b)</b> Write a short note on cross over distortion.	<b>04</b>
	<b>(c)</b> Explain the working of summing amplifier and averaging amplifier when connected in Inverting mode.	<b>07</b>
	<b>OR</b>	
	<b>(c)</b> Draw the circuit Op-Amp as a Integrator and explain with necessary waveforms.	<b>07</b>
<b>Q.3</b>	<b>(a)</b> How to rectify stability and high frequency noise problem in a basic differentiator?	<b>03</b>
	<b>(b)</b> Explain the operation of Zero crossing detector.	<b>04</b>
	<b>(c)</b> Draw and explain Wien Bridge Oscillator.	<b>07</b>
	<b>OR</b>	
<b>Q.3</b>	<b>(a)</b> Compare the inverting and non-inverting comparators.	<b>03</b>
	<b>(b)</b> With the help of circuit diagram explain the working of Schmitt Trigger.	<b>04</b>
	<b>(c)</b> With the help of circuit diagram explain voltage to current convertor with it's application.	<b>07</b>
<b>Q.4</b>	<b>(a)</b> Define : 1)Pass band 2)Cut of frequency 3)Attenuation	<b>03</b>
	<b>(b)</b> Derive the out put voltage equation of basic differentiator.	<b>04</b>
	<b>(c)</b> Explain with circuit diagram the operation of VCO.	<b>07</b>
	<b>OR</b>	
<b>Q.4</b>	<b>(a)</b> Compare Active Filter and Passive Filter.	<b>03</b>
	<b>(b)</b> Compare Astable , Monostable and Bistable Multivibrator	<b>04</b>
	<b>(c)</b> Draw and explain basic block schematic of 79XX series three terminal voltage regulator ICs.	<b>07</b>
<b>Q.5</b>	<b>(a)</b> Explain Butterworth response	<b>03</b>
	<b>(b)</b> List advantages and disadvantages of adjustable voltage regulators.	<b>04</b>
	<b>(c)</b> Explain the working of IC 555 as a Astable Multivibrator.	<b>07</b>
	<b>OR</b>	
<b>Q.5</b>	<b>(a)</b> What is the effect of negative feedback on gain & bandwidth?	<b>03</b>
	<b>(b)</b> Describe the operation of a LM 317 voltage regulator.	<b>04</b>
	<b>(c)</b> Explain the working of PLL using appropriate block diagram	<b>07</b>

\*\*\*\*\*