

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER– IV (New) EXAMINATION – WINTER 2019****Subject Code: 2141003****Date: 12/12/2019****Subject Name: Electronics Measurement and Instrumentation****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		<b>MARKS</b>
<b>Q.1</b>	(a) Define: (1) Accuracy (2) Precision (3) Resolution	<b>03</b>
	(b) Explain: (1) Gross errors (2) Random errors.	<b>04</b>
	(c) Describe the classification of standards in detail	<b>07</b>
<b>Q.2</b>	(a) Explain the applications and limitations of Wheatstone bridge.	<b>03</b>
	(b) Draw the circuit diagram of Kelvin bridge and derive the equation for unknown resistance.	<b>04</b>
	(c) Draw the circuit diagram of Maxwell's bridge and derive the equation for unknown Inductance and resistance. What are its advantages and disadvantages?	<b>07</b>
<b>OR</b>		
	(c) Draw the circuit diagram of Hay's bridge and derive the equation for unknown Inductance and resistance. What are its advantages and disadvantages?	<b>07</b>
<b>Q.3</b>	(a) Draw the circuit diagram of de-sauty's bridge and derive the equation for unknown Capatance.	<b>03</b>
	(b) Draw the circuit diagram of Schering's bridge and derive the equation for unknown Capatance and resistance.	<b>04</b>
	(c) An unbalanced Wheatstone bridge has following details: $R_1=1K, R_2=2.5K, R_3=3.5K, R_4=10K, R_G=300\Omega$ , battery $E=6V$ . Calculate the current through the Galvanometer.	<b>07</b>
<b>OR</b>		
<b>Q.3</b>	(a) A Maxwell bridge is used to measure inductive impedance. The bridge constants are: $C_1=0.01\mu F, R_1=470k\Omega, R_2=5.1k\Omega, R_3=100k\Omega$ Find the series equivalent of the unknown impedance.	<b>03</b>
	(b) Draw the diagram of digital frequency meter and explain its working.	<b>04</b>
	(c) Find the series equivalent inductance and resistance of hay's bridge to null with the following bridge arms( clockwise ABCD): Arm AB: $R_1=2k\Omega, C_1=1\mu F$ , Arm BC: $R_3=1k\Omega$ , Arm CD: unknown $R_x$ and $L_x$ Arm DA: $R_2=10k\Omega$ $\omega=3000$ rad/s	<b>07</b>
<b>Q.4</b>	(a) Draw the block diagram of a pulse generator. (only diagram, no description)	<b>03</b>

- (b) Draw the block diagram of standard signal generator and explain its operation. **04**
- (c) Draw the circuit diagram of Wien's bridge and derive the equation for unknown frequency. **07**
- OR**
- Q.4** (a) Draw the block diagram of sweep generator. **03**  
(only diagram, no description).
- (b) Draw the block diagram of AF sine and square wave generator and explain its working briefly. **04**
- (c) Draw the block diagram of true rms reading volt meter and explain its working in detail. What are its advantages and disadvantages? **07**
- Q.5** (a) Draw the circuit diagram of basic wave analyzer and explain its working briefly. **03**
- (b) Draw the block diagram of function generator and explain its operation. **04**
- (c) Draw the block diagram of basic CRO and explain the function of each block. **07**
- OR**
- Q.5** (a) Draw the basic construction of linear variable differential transducer(LVDT) and explain its working briefly. **03**
- (b) With diagram explain the working principle of spectrum analyzer. **04**
- (c) Draw the block diagram of digital storage oscilloscope and explain its principle of operation in detail. **07**