

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE- SEMESTER-III (NEW) EXAMINATION – WINTER 2020****Subject Code:3132003****Date:04/03/2021****Subject Name:Design Concepts in Basic Electronics****Time:10:30 AM TO 12:30 PM****Total Marks:56****Instructions:**

1. Attempt any **FOUR** questions out of **EIGHT** questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Compare Digital System with Analog System in terms of their pros and cons. **03**  
 (b) Give detail comparison of half-wave and full-wave rectifiers. **04**  
 (c) Explain the collector feedback biasing with emitter resistance in details. **07**
- Q.2** (a) Explain basic Gates with their truth tables. **03**  
 (b) Derive the equations of  $I_{DC}$ ,  $V_{DC}$ ,  $I_{RMS}$ ,  $V_{RMS}$  and PIV for full wave bridge rectifier. **04**  
 (c) Explain NAND Gate as universal Gate. **07**
- Q.3** (a) A diode in series with resistor of  $220\Omega$ . If the voltage across the diode is 6 V, what is the current through the diode? **03**  
 (b) Construct  $3 \times 8$  Decoder. **04**  
 (c) Explain forward bias and reverse bias V-I Characteristics for PN junction diode. **07**
- Q.4** (a) What is barrier potential? Explain the effect of temperature on barrier potential. **03**  
 (b) Simplify the Boolean Expression and implement the circuit using minimum number of Logic Gates. **04**
- $$A[\overline{(\overline{A + B})C + \overline{AB}}]$$
- (c) Attempt the following; **07**
1. Express  $(-53)_{10}$  as 8 bit binary number using sign magnitude.
  2.  $(CA7)_{16} = (\text{_____})_2$ .
  3.  $(1011)_2 - (110)_2 = \text{_____}$ .
  4. What is 2's complement of binary number 11010101?
  5. Convert 269 decimal number to octal number by repeated division by 8 method.
  6. IC 7404 is for \_\_\_\_\_ Gate.
  7.  $A+AB = \text{_____}$ .
- Q.5** (a) Compare combinational circuits with sequential circuits. **03**  
 (b) Explain biased negative clamper circuit. **04**  
 (c) Simplify the following function using Karnaugh map method. Also implement the circuit for minimized function using logic gates. **07**
- $$F(A, B, C, D) = \sum\{1,2,3,5,7,9,10,11,13,14\}$$
- Q.6** (a) Draw discrete circuits for AND Gate and OR Gate using Transistor-Transistor logic. **03**  
 (b) Explain the negative clamper with circuit diagram. **04**  
 (c) Simplify the following function using Karnaugh map method. Also implement the circuit for minimized function using logic gates. **07**
- $$F(A, B, C, D) = \Pi\{0,2,3,5,9,10,12,15\}$$
- Q.7** (a) Explain Gated S-R Latch with waveforms. **03**

- (b) Design and explain 2-Bit Asynchronous (Ripple) Counter. **04**
- (c) What are the configuration which increases the stability of Q-Point and explain any one of it. **07**
- Q.8** (a) Explain Serial-In/Serial-Out shift register. **03**
- (b) Design 1-Bit magnitude comparator. **04**
- (c) Explain the Ideal, Second and Third approximation for diode in detail with example. **07**

\*\*\*\*\*