

GUJARAT TECHNOLOGICAL UNIVERSITY

BE- SEMESTER-III (NEW) EXAMINATION – WINTER 2020

Subject Code:3134104

Date:05/03/2021

Subject Name:Electronic Devices and Circuits


Time:10:30 AM TO 12:30 PM

Total Marks:56


Instructions:

1. Attempt any FOUR questions out of EIGHT questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		Marks
Q.1	(a) What is doping in semiconductor material?	03
	(b) How the depletion layer is formed in unbiased diode?	04
	(c) Draw half wave rectifier circuit. Draw waveform for voltage across diode, diode current with R and RC load.	07
Q.2	(a) Compare Zener Diode and PN junction Diode.	03
	(b) Write a short note on Varactor diode.	04
	(c) Explain capacitive filter with Ripple Factor.	07
Q.3	(a) Explain transistor construction with size and doping level of each region.	03
	(b) Differentiate FET and BJT.	04
	(c) For the fixed-bias circuit shown, determine	07
	(i) Collector current, I_C	
	(ii) Collector resistance, R_C	
	(iii) Base resistance, R_B	
	(iv) VCE.	
	Assume $\beta = 80$ and $V_{BE} = 0.7 \text{ V}$.	

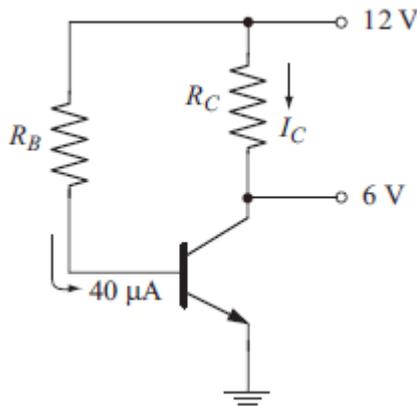

Q.4	(a) How transistor act as a switch? What are limitations?	03
	(b) Draw V-I characteristics of Zener diode.	04
	(c) What value should R_2 be in figure below to set up a diode current of 0.25 mA? Consider $V_D=0.7\text{v}$	07

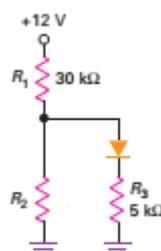

Q.5	(a) Describe the purpose of cascading CE and CC amplifiers.	03
	(b) Explain the T Model of a transistor.	04
	(c) Explain the voltage divider bias circuit in detail.	07
Q.6	(a) What is the use of Heat Sinks in power amplifier?	03
	(b) Explain the difference of class A and class B operation of an amplifier.	04
	(c) Draw and explain class B push-pull amplifier.	07
Q.7	(a) List the advantages of Negative feedback.	03
	(b) Describe JFET applications as analog switch.	04
	(c) Explain Darlington pair connections of two transistors.	07
Q.8	(a) Summarize all four negative feedback amplifier with input output resistance and voltage gain.	03
	(b) Compare FET with BJT.	04
	(c) Explain construction, operation and characteristic of P-channel Enhancement type MOSFET in detail.	07
