

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III (NEW) EXAMINATION – WINTER 2021****Subject Code:3132003****Date:21-02-2022****Subject Name:Design Concepts in Basic Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

- Q.1** (a) Differentiate between analog system and digital system. **03**
- (b) Explain the Base Curve for common emitter configuration. **04**
- (c) Attempt the following: **07**
1. Perform binary addition for numbers $(10111)_2$ and $(01011)_2$.
 2. $(AF2)_{16} = (\quad)_2$.
 3. $(001011)_2 = (\quad)_8$.
 4. What is 1's complement of binary number 10011011?
 5. Convert decimal number 356 to BCD number.
 6. Convert $(101100111)_2$ to Grey code.
 7. $A+A = \quad$ as per Boolean algebra.
- Q.2** (a) Explain forward bias condition for PN junction diode. **03**
- (b) Explain edge triggered SR flip-flop with waveforms. **04**
- (c) Explain significance of digital system with block diagram. **07**
- OR**
- (c) Explain NOR Gate as universal Gate. **07**
- Q.3** (a) Explain positive bias series clipper with circuit diagram and waveform. **03**
- (b) Briefly explain intrinsic material and extrinsic material. **04**
- (c) Give detail explanation of Ideal, Second and Third approximation for Transistor. **07**
- OR**
- Q.3** (a) Prove $(A+B)(A+C) = A+BC$ using Boolean algebra. **03**
- (b) Explain error detection using parity bit. **04**
- (c) Explain AND Gate, OR Gate and NOT Gate in detail with their truth tables and discrete circuits based on TTL. **07**
- Q.4** (a) Explain Voltage Tripler circuits with circuit diagram. **03**
- (b) Derive the equations of I_{DC} , V_{DC} , I_{RMS} and V_{RMS} for full wave bridge rectifier. **04**
- (c) Explain half wave and full wave rectifiers with circuit diagrams and wave forms. **07**

OR

- Q.4** (a) Simplify $[A(B+C)'+A'(B+C)']'$ using Boolean Algebra. **03**
- (b) Use the K-map to minimize the following SOP expression and find its binary value. **04**
- $AB'C + A'BC + A'B'C + A'B'C' + AB'C'$
- (c) Design and explain Serial In/Serial Out Shift Register. **07**
- Q.5** (a) Explain 4×1 Multiplexer. **03**
- (b) Express the Boolean Function $F = (X'+Y)(X+Z)(Y+Z)$ in a product of maxterm. The Function has three variable X, Y and Z. **04**
- (c) Design and explain 2-bit Magnitude Comparator. **07**

OR

- Q.5** (a) A diode in series with resistor of 200Ω . If the voltage across the diode is 8 V, calculate the current through the diode. **03**
- (b) Explain biased negative clamper circuit. **04**
- (c) Explain emitter feedback bias for transistor. **07**
