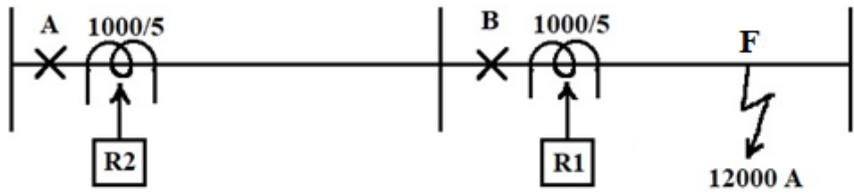


GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VII (NEW) EXAMINATION – WINTER 2021****Subject Code:3170908****Date:10/12/2021****Subject Name:Switchgear And Protection****Time:10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

- Q.1** (a) What do you understand by 30° and 60° connections with reference to directional overcurrent relays? **03**
- (b) The percentage differential protection of transformer will not operate during an external fault. Explain and justify with suitable figure. **04**
- (c) What do you understand by a zone of protection? Discuss various zones of protection for a modern power system. Why do adjacent protective zones overlap? **07**
- Q.2** (a) Explain the effect of arc resistance on Mho relay reach and the directional property of Mho relay with the help of characteristics on R-X plane. **03**
- (b) Explain capacitor voltage transformer. Give its comparison with electromagnetic potential transformer. **04**
- (c)  **07**

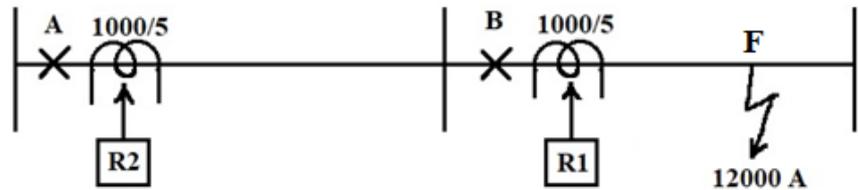


Figure 1

Two relays R_1 and R_2 are connected in two sections of a feeder, with CT ratios of 1000/5 A as shown in Figure 1 above. The plug settings of relay R_1 and R_2 are 150% and 200% respectively. Operating time characteristic of both relays at TMS=1 is given in Table 1 below.

Table 1

PSM	2	4	5	6	8	10	12	15	20
Operating Time (s)	10	5	4	3.6	3	2.8	2.6	2.2	1.6

The time multiplier setting of relay R_1 is 0.3. The time grading scheme has a discriminative time margin of 0.5 seconds between the relays. A three-phase short circuit at F results in a fault current as shown in figure.

Find the actual operating times of R_1 and R_2 .

What is the time multiplier setting of R_2 ?

OR

- (c) With suitable waveforms, explain the problem of magnetizing inrush in case of transformer protection. Explain how percentage differential relay with harmonic restraint can overcome this problem. **07**

- Q.3** (a) Briefly explain how the CT ratio should be selected for differential protection of bus-bars. **03**
- (b) Explain in brief selectivity, sensitivity, discrimination and speed with reference to protective relaying. **04**
- (c) In relation to circuit breaker arc interruption, explain the recovery rate theory and energy balance theory. Also with suitable figure, define restriking voltage and recovery voltage. **07**

OR

- Q.3** (a) What is back up protection and why is it needed? **03**
- (b) Explain the necessity of directional overcurrent relay in case of single end fed parallel feeders and radial feeders. **04**
- (c) Compare Air Blast Circuit Breaker, SF₆ Circuit Breaker and Vacuum Circuit Breaker with reference to their arc quenching mechanisms. **07**

- Q.4** (a) Briefly explain various types of faults and abnormal conditions in transformers. **03**
- (b) Explain unbalanced loading and loss of excitation as abnormal operating condition of alternator. **04**
- (c) With the help of characteristics on R-X plane, compare between performance of impedance and reactance relays in terms of: i) Directional property exhibited by the relay; ii) Performance of relay during power swing. **07**

OR

- Q.4** (a) Explain the difference between CT cores used for measurement and those used for protective relays. **03**
- (b) Explain three stepped distance protection of transmission line. **04**
- (c) Explain the basic schematic of differential protection of bus-bars. Explain its behavior with reference to internal and external faults, clearly explaining the reason of maloperation during external faults. **07**

- Q.5** (a) Explain the concept of adaptive relaying. **03**
- (b) Explain how to select short-time current rating of CT and accuracy class of CT while selecting a CT. **04**
- (c) With schematic, explain protection from phase fault and ground fault inside the three phase induction motor. **07**

OR

- Q.5** (a) Explain the problem associated with unbalanced supply voltage and the method of protection from the same for a three phase induction motor. **03**
- (b) Draw and explain the general block diagram of numerical relay. **04**
- (c) List out various stator and rotor faults of generator. Explain transverse differential protection of generator winding. **07**
