

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY
BE - SEMESTER-I & II(NEW) EXAMINATION – WINTER 2022

Subject Code:2110005

Date:13-03-2023

Subject Name:Elements of Electrical Engineering

Time:10:30 AM TO 01:00 PM

Total Marks:70

Instructions:

- 1. Question No. 1 is compulsory. Attempt any four out of remaining Six questions.**
- 1. Make suitable assumptions wherever necessary.**
- 2. Figures to the right indicate full marks.**
- 3. Simple and non-programmable scientific calculators are allowed.**

- | | | |
|------------|--|-------------|
| Q.1 | Choose the correct option from the given options | Mark |
| (a) | | 07 |
| 1. | The three resistors of resistance values 5Ω , 10Ω , and 15Ω are connected in parallel, what should be its equivalent resistance
(a) Less than 5Ω (b) between 5Ω and 10Ω (c) between 10Ω and 15Ω (d) greater than 15Ω | |
| 2. | Kirchhoff's voltage law is concerned with
(a) IR drops (b) battery e. m. f. (c) junction voltages (d) both (a) & (b) | |
| 3. | The resistance of each arm of delta connected network 6Ω . The resistance of each arm of its equivalent star connected network is
(a) 6Ω (b) 18Ω (c) 2Ω (d) 3Ω | |
| 4. | A capacitor that stores a charge of 0.5 C at 10 V has capacitance of _____ farad.
(a) 5 (b) 0.05 (c) 20Ω (d) 0 | |
| 5. | The SI unit of electric field intensity is
(a) N/m (b) V/m (c) N/C (d) either (b) or (c) | |
| 6. | According to Faraday's law of electromagnetic induction, an e. m. f. is induced in a conductor whenever it
(a) lies in a magnetic field (b) cuts magnetic flux (c) moves parallel to the direction of the magnetic field (d) lies parallel to the magnetic flux | |
| 7. | A coil of 1000 turns is wound on a core. A current of 1 A flowing through the coil creates a core flux of 1 mWb . The energy stored in the magnetic field is
(a) 0.25 J (b) 0.5 J (c) 1 J (d) 2 J | |
| (b) | | 07 |
| 1. | The power factor of series R-L-C circuit under resonance condition is
(a) 0.8 lagging (b) unity (c) zero (d) 0.8 leading | |
| 2. | An AC current given by $i=14.14\sin(\omega t + \pi/6)$ has an r. m. s. value of _____ A
(a) 7.07 (b) 1.96 (c) 10 (d) 14.14 | |
| 3. | The voltage applied across an R-L series circuit is equal to
(a) arithmetic sum of V_R and V_L (b) algebraic sum of V_R and V_L (c) phasor sum of V_R and V_L (d) sum of squares of V_R and V_L | |
| 4. | The minimum number of wattmeter(s) required to measure 3-phase, 3-wire balanced or unbalanced power is
(a) 4 (b) 2 (c) 3 (d) 1 | |
| 5. | The rating of the battery is
(a) Ah (b) kWh (c) W (d) hp | |
| 6. | Fuse provides protection against
(a) over load (b) short circuit (c) both (a) & (b) (d) lightning | |
| 7. | Which of the following provides safety to human against electric shock
(a) RELAY (b) FUSE (c) MCB (d) earthing | |

- Q.2** (a) Write the statements of Kirchoff's law **03**
 (b) Give difference between dependent and independent sources. **04**
 (c) Find the current through the 2Ω resistor shown in figure 1 by using loop analysis. **07**

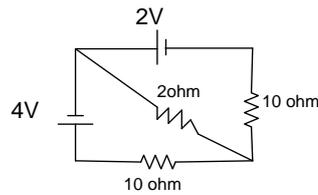


Figure 1

- Q.3** (a) Write the laws of electrostatics **03**
 (b) Derive the expression of energy stored in capacitor. **04**
 (c) Explain the statically and dynamically induced e. m. f. **07**
- Q.4** (a) State Fleming's and Lenz's laws **03**
 (b) Explain hysteresis loop. **04**
 (c) Find the charges on capacitor C_1 , C_2 and C_3 shown in figure 2. **07**

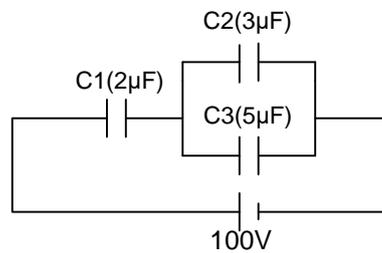


Figure 2

- Q.5** (a) Explain form factor and peak factor for a sinusoidal waveform. **03**
 (b) Explain real power, reactive power and apparent power in ac circuit. **04**
 (c) A pure resistance of 50 ohms is in series with a pure capacitance of 100 microfarads. The series combination is connected across 100-V, 50Hz supply. Determine (a) the impedance (2) current (3) power factor (4) phase angle (5) voltage across the resistor (6) voltage across the capacitor. **07**
- Q.6** (a) What is the difference between balanced and unbalanced three phase load. **03**
 (b) Write short note on CFL and LED lamps. **04**
 (c) The power in a 3-phase circuit is measured by two wattmeters. If the total power is 100KW and power factor is 0.66 leading. What will be the reading of each wattmeter? **07**
- Q.7** (a) State the safety precautions to be taken in home to prevent electric shock. **03**
 (b) Explain plate earthing with figure. **04**
 (c) Explain ELCB in details. **07**
