

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER- III(NEW) EXAMINATION – WINTER 2022****Subject Code:3132003****Date:24-02-2023****Subject Name:Design Concepts in Basic Electronics****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

- Q.1**
- (a) Differentiate between analog and digital system. **03**
- (b) Explain De-Morgan's theorem with suitable examples. **04**
- (c) Attempt the following questions: **07**
1. Perform binary division of 110 by 10.
 2. Find 1's complement of 10111001.
 3. Express $(-19)_{10}$ as 8 bit binary number using sign magnitude.
 4. Convert $(531)_{10}$ to its equivalent BCD number.
 5. Convert $(010101)_2$ to Octal number.
 6. $(3F1)_{16} = (\text{_____})_2$.
 7. Convert binary number 10110 to grey code.
- Q.2**
- (a) Explain working of series positive clipper with circuit diagram and waveforms. **03**
- (b) Draw the logic diagrams corresponding to the following Boolean expressions **04**
without simplifying them.
1. $(A+C)(A+D)(A'+C+D)$
 2. $A'B+ACD+BD'$
- (c) With circuit diagram and waveforms explain working of D flip-flop. **07**
- OR**
- (c) Explain emitter feedback bias for transistor. **07**
- Q.3**
- (a) Differentiate between combinational circuits and sequential circuits. **03**
- (b) Explain full-wave voltage doubler circuit with application. **04**
- (c) Simplify the following Boolean expression to minimum number of literals and implement it with logic Gates. **07**
- $$A[B+C'(AB+AC)']$$
- OR**
- Q.3**
- (a) Explain reverse bias condition for PN junction diode. **03**
- (b) Define RTL, TTL, ECL and CMOS. **04**
- (c) Explain different types of logic Gates with their functions and truth tables. **07**
- Q.4**
- (a) Explain significance of rectifier with one application. **03**
- (b) Express the following functions in sum of minterms and product of maxterms. **04**
1. $F(A, B, C) = (A'+B)(A+C)(B+C')$
 2. $F(X, Y, Z) = XY'+Y'Z+XZ$
- (c) Design BCD to Seven segment decoder. **07**

OR

- Q.4** (a) Explain the effect of temperature on barrier potential. **03**
(b) Design combinational circuits for half adder and half subtractor. **04**
(c) Explain working of 4-bit ripple counter with diagram. **07**

- Q.5** (a) Explain the capacitor input filter for half wave rectifier. **03**
(b) Briefly explain Q-point for a transistor. **04**
(c) Explain bidirectional shift register with parallel load. **07**

OR

- Q.5** (a) Explain conduction band and valence band. **03**
(b) Explain the ideal and second approximation for diode in detail with example. **04**
(c) Explain the input and output characteristic of common emitter configuration of transistor. **07**
