

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**BE - SEMESTER-VII (NEW) EXAMINATION – WINTER 2022**

**Subject Code:3172413**

**Date:05-01-2023**

**Subject Name:Advanced Power Electronics Devices and Interface Circuits**

**Time:10:30 AM TO 01:00 PM**

**Total Marks:70**

**Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
<b>Q.1</b>	(a) Explain concept of Wide Band Gap (WBG) power semiconductor devices.	<b>03</b>
	(b) Give the comparison of WBG (SiC, GaN) and Si devices.	<b>04</b>
	(c) Explain any half bridge driver IC.	<b>07</b>
<b>Q.2</b>	(a) Discuss grounding considerations for driver circuits.	<b>03</b>
	(b) Discuss requirement & importance of isolation.	<b>04</b>
	(c) Explain any half bridge driver IC with SC Protection.	<b>07</b>
<b>OR</b>		
	(c) Explain single switch driver IC in detail. (e.g., TLP250)	<b>07</b>
<b>Q.3</b>	(a) Explain galvanic isolation.	<b>03</b>
	(b) Explain importance of various protection.	<b>04</b>
	(c) Write short note on hall effect current sensor.	<b>07</b>
<b>OR</b>		
<b>Q.3</b>	(a) Discuss current transformer.	<b>03</b>
	(b) Explain force to voltage converter.	<b>04</b>
	(c) Explain SCR driver IC (MOC3002) in detail.	<b>07</b>
<b>Q.4</b>	(a) List out applications of Logic Analyzer.	<b>03</b>
	(b) Discuss thermal resistance & its Consideration.	<b>04</b>
	(c) Draw and explain block diagram of oscilloscope.	<b>07</b>
<b>OR</b>		
<b>Q.4</b>	(a) List our various cooling methods.	<b>03</b>
	(b) Explain forced and natural cooling of heat sinks.	<b>04</b>
	(c) Explain heat sink calculations and design in detail.	<b>07</b>
<b>Q.5</b>	(a) Explain linear opto-coupler.	<b>03</b>
	(b) Discuss transformer design for driver circuits.	<b>04</b>
	(c) Describe general steps to inductor design for power converters.	<b>07</b>
<b>OR</b>		
<b>Q.5</b>	(a) Discuss considering of grounding for Power Circuits.	<b>03</b>
	(b) Explain the use of differential voltage probe.	<b>04</b>
	(c) Explain transformer design for “Forward Converter” in detail.	<b>07</b>

\*\*\*\*\*