

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III (NEW) EXAMINATION – WINTER 2023

Subject Code:2130902

Date:18-01-2024

Subject Name:Analog Electronics

Time:10:30 AM TO 01:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

| | | MARKS |
|---|--|-----------|
| Q.1 | (a) Briefly explain block-diagram representation of op-amp. | 03 |
| | (b) List the advantages of negative feedback in amplifiers. | 04 |
| | (c) Explain in detail class B push pull power amplifier with circuit diagram. | 07 |
| Q.2 | (a) What is the effect of negative feedback on bandwidth? Explain briefly. | 03 |
| | (b) Define following: (1) PSRR (2) CMRR (3) Input bias current (4) Gain-Bandwidth product | 04 |
| | (c) Explain in detail closed-loop differential amplifier with one op-amp. | 07 |
| | OR | |
| (c) Explain in detail JFET amplifier in common drain configuration. | 07 | |
| Q.3 | (a) List out the characteristics of ideal op-amp. | 03 |
| | (b) Draw and explain equivalent circuit of op-amp. | 04 |
| | (c) Write a short-note on summing, scaling and averaging amplifier in inverting mode. | 07 |
| OR | | |
| Q.3 | (a) Draw and explain voltage-to-current converter circuit with grounded load. | 03 |
| | (b) Write a short-note on the peaking amplifier. | 04 |
| | (c) Define input offset and output offset voltages. Draw and explain the offset null circuit for op-amp 741. | 07 |
| Q.4 | (a) Write a short-note on Slew rate along with effect of slew rate in applications. | 03 |
| | (b) Briefly explain: (i) Open-loop inverting amplifier (ii) Open-loop non-inverting amplifier. | 04 |
| | (c) Write a short-note on second-order low-pass butterworth filter. | 07 |
| | OR | |
| Q.4 | (a) State the advantages of active filters over passive filters? | 03 |
| | (b) Describe the operation of a LM 317 voltage regulators. | 04 |
| | (c) Explain the practical integrator circuit with diagram and waveforms. | 07 |

- Q.5** (a) Compare positive and negative feedbacks for amplifiers. **03**
(b) Draw the neat sketch of Schmitt Trigger circuit and explain how it works. **04**
(c) Explain the working of IC 555 as an astable multivibrator. **07**
- OR**
- Q.5** (a) Briefly explain the block diagram of 555 timer IC. **03**
(b) Draw and discuss block diagram of PLL. **04**
(c) Draw and explain instrumentation amplifier using op-amp. **07**
