

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III (NEW) EXAMINATION – WINTER 2023

Subject Code:3131704

Date:12-01-2024

Subject Name:Digital Electronics

Time:10:30 AM TO 01:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

	MARKS
Q.1 (a) Explain binary, octal and hexadecimal number system with example.	03
(b) Briefly explain combinational circuit and sequential circuit.	04
(c) List out various logic gates and explain each with proper diagram and truth table.	07
Q.2 (a) What is gray code? Explain in brief.	03
(b) Convert the following numbers to decimal numbers	04
1) (1010.011) ₂ 2) (630.4) ₈	
(c) Explain basic theorems and properties of Boolean Algebra.	07
OR	
(c) Briefly explain Minterms and Maxterms with example.	07
Q.3 (a) Explain De'Morgan's theorem.	03
(b) Convert the following numbers to assigned number system	04
1) 153 to Octal 2) (0.6875) to Binary	
(c) Express the following Boolean function in the product of Maxterm form: $F = xy + x'z$	07
OR	
Q.3 (a) Explain the concept of Venn Diagram.	03
(b) Design a half adder circuit using proper equations and truth table.	04
(c) Simplify the Boolean function using K map.	07
$F(x,y,z) = \sum (0,2,4,5,6)$	
Q.4 (a) Briefly explain Multiplexer.	03
(b) Explain NAND Gate as a universal gate.	04
(c) Explain J-K Flip Flop in detail.	07
OR	
Q.4 (a) Briefly explain De Multiplexer.	03
(b) Explain NOR Gate as a universal gate.	04
(c) Explain Master- Slave Flip Flop in detail.	07
Q.5 (a) Explain the following terms	03
1) Propagation Delay 2) Fan in 3) Fan out	
(b) Explain Register and Shift Register in detail.	04
(c) What is DTL circuit? Explain any one DTL circuit for logic gate.	07

OR

- Q.5** (a) Explain the following terms **03**
1) Threshold Voltage 2) Noise Margin 3) Power Dissipation
- (b) Explain types of memories in detail. **04**
- (c) What is TTL circuit? Explain any one TTL circuit for logic gate. **07**
