

GUJARAT TECHNOLOGICAL UNIVERSITY**BE- SEMESTER-III (NEW) EXAMINATION – WINTER 2024****Subject Code: 3131704****Date: 21-11-2024****Subject Name: Digital Electronics****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) Show how a full adder can be converted to a full subtractor with the help of inverter circuit.	03
	(b) Convert the following numbers into binary.	04
	(i) $(25.8)_{10}$	
	(ii) $(47FD)_{16}$	
	(iii) $(573.2)_8$	
	(c) Simplify the Boolean function F using don't care conditions d, in (i) sum of products and (ii) product of sums $F = w'(x'y + x'y' + xyz) + x'z'(y + w)$ $d = w'x(y'z + yz') + wyz$	07
Q.2	(a) What do you mean by reflected code? Show one of the possible combination of 4-bit reflected code.	03
	(b) Explain standard and canonical forms along with example.	04
	(c) Design a combinational circuit for BCD to excess-3 code converter.	07
	OR	
	(c) Explain clocked RS flip-flop with circuit diagram and truth table. Also discuss about limitation of RS flip-flop.	07
Q.3	(a) Construct a 4 x 16 decoder with 3x 8 decoder.	03
	(b) Differentiate between	04
	(i) Combination and sequential circuits	
	(ii) Edge triggered and level triggered flip-flop	
	(c) Explain the 4-bit magnitude comparator with necessary diagrams and equations.	07
	OR	
Q.3	(a) Implement NOT, AND & OR gates with the help of NAND gate.	03
	(b) Explain Master-Slave flip-flop.	04
	(c) Explain bus system for four registers.	07
Q.4	(a) Prove the following Boolean expression using Boolean algebra simplification. $BC + AC' + AB + BCD = BC + AC'$	03
	(b) Explain TTL gate with Totem-pole output	04
	(c) Explain ring counter in detail.	07
	OR	

- Q.4 (a)** Represent the decimal number 8620 in **03**
- (i) BCD
- (ii) Excess-3 code
- (iii) 5421 code
- (b)** Express the following function in a sum of minterms and a product of maxterms. **04**
- $F(A, B, C, D) = D(A' + B) + B'D$
- (c)** Explain 4-bit bidirectional shift register with parallel load. **07**
- Q.5 (a)** Explain the working of JK flip-flop. **03**
- (b)** Define **04**
- (i) Fan-out
- (ii) Power Dissipation
- (iii) Propagation delay
- (iv) Noise Margin
- (c)** Design 3-bit Binary counter with T flip-flops. **07**
- OR**
- Q.5 (a)** Explain Macro-operations versus Micro-operations. **03**
- (b)** Explain arithmetic and logic micro-operations. **04**
- (c)** Design BCD counter with T flip-flops. **07**
