

GUJARAT TECHNOLOGICAL UNIVERSITY**BE- SEMESTER-III (NEW) EXAMINATION – WINTER 2024****Subject Code:3134104****Date:10-12-2024****Subject Name: Electronic Devices and Circuits****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

Q.1*	(a)	Explain Energy Hill.	03
	(b)	Draw & Explain Energy Band diagram for Conductor, Insulator and Semiconductor	04
	(c)	Explain Full wave Bridge Rectifier with its circuit diagram and waveforms	07
Q.2	(a)	Draw and explain third approximation of Diode.	03
	(b)	Explain How to calculate the bulk resistance in PN junction diode.	04
	(c)	Explain DC load line for PN junction diode with circuit diagram, waveforms and necessary calculations.	07
		OR	
	(c)	Explain Positive and Negative Clipper using its circuit diagram and wave forms.	07
Q.3	(a)	Compare Zener Breakdown and Avalanche Breakdown	03
	(b)	Explain Varactor Diode.	04
	(c)	Explain Zener diode as a voltage regulator.	07
		OR	
Q.3	(a)	Draw and explain the collector curves with indication of its 03 regions.	03
	(b)	Derive the relation between DC α (alpha) and DC β (beta) for BJT.	04
	(c)	Explain Transistor as a Switch, and also its limitations as a switch.	07
Q.4	(a)	Explain Optocoupler.	03
	(b)	Explain frequency response of an Amplifier.	04
	(c)	Explain Emitter biasing method for Transistor Biasing.	07
		OR	
Q.4	(a)	Explain two Transistor Model in AC biasing of Transistor	03
	(b)	Explain Collector feedback bias method for transistor biasing.	04
	(c)	Explain Class A amplifier with its circuit diagram and waveforms.	07
Q.5	(a)	Explain Class C operation with circuit and waveforms.	03
	(b)	Explain Transconductance curves for JFET.	04
	(c)	Explain construction and operating principle for N Channel Enhancement type MOSFET	07

OR			
Q.5	(a)	Compare JFET and MOSFET.	03
	(b)	Explain Method of identifying the feedback topology.	04
	(c)	Explain effect of Negative Feedback in Amplifier characteristics.	07
