

GUJARAT TECHNOLOGICAL UNIVERSITY

BE- SEMESTER-VII (NEW) EXAMINATION – WINTER 2024

Subject Code:3172413

Date:07-12-2024

Subject Name: Advanced Power Electronics Devices and Interface Circuits

Time:10:30 AM TO 01:00 PM

Total Marks:70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

	MARKS
Q.1 (a) What is logic analyzer? State its applications.	03
(b) Discuss requirement of isolation for driver circuit design.	04
(c) What are wide band gap materials? What are their advantages over other semiconductors?	07
Q.2 (a) Can pulse transformer be used for driving IGBT ? Justify your answer.	03
(b) Explain MOC203x TRIAC driver IC with its internal diagram.	04
(c) Explain half bridge driver circuit using IR2110 IC.	07
OR	
(c) Explain application of TLP250 driver IC with necessary diagrams.	07
Q.3 (a) List various shapes of core used for transformer design.	03
(b) Explain opto-coupler driver IC MCT 2E as driver of single semiconductor switch.	04
(c) Explain step by step procedure for transformer design.	07
OR	
Q.3 (a) Which material is suitable for high frequency inductor design? Why?	03
(b) Explain LM331 IC for F to V conversion application.	04
(c) Discuss hall effect current sensor for current measurement.	07
Q.4 (a) Give advantages of power scope.	03
(b) What are differential probes? Explain its application.	04
(c) Explain various thermal coefficients related to heat sink design.	07
OR	
Q.4 (a) How many isolated power supplies are required for single phase full bridge inverter driver circuits. Justify your answer.	03
(b) Describe current probe in brief.	04
(c) Discuss various protections available with modern driver ICs.	07
Q.5 (a) Explain any type of ADC in brief.	03
(b) Explain forced cooling of heat sink.	04
(c) Derive equation of inductor for buck converter.	07
OR	
Q.5 (a) Why ADC is required in reference to driver circuit design.	03
(b) How current could be measured with the help of voltage probe?	04
(c) Derive equation of inductor for boost converter.	07
