

GUJARAT TECHNOLOGICAL UNIVERSITY
M.SC(IT)- INTEGRATED – SEMESTER III- EXAMINATION –WINTER-2024

Subject Code:1330504**Date: 28/11/2024****Subject Name: Digital Electronics****Time:10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make Suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		Marks
Q.1	(a) Convert (i) $(110101)_2$ to decimal number and (ii) $(673.124)_8$ to binary number	03
	(b) (i) By using 10's complement subtract $72532 - 3250$ (ii) By using 1's complement subtract $1010100-1000011$	04
	(c) Define binary logic. Explain Binary-Coded Decimal (BCD) code.	07
Q.2	(a) State the DeMorgan's theorem and validate it by using truth table.	03
	(b) Find the complement of the functions $F_1 = x'yz' + x'y'z$ and $F_2 = x(y'z'+yz)$ by taking their duals and complementing each literal.	04
	(c) Prepare a truth table for $F = x'y'z + x'yz + xy'$ and implement it with the logic gates.	07
OR		
	(c) Simplify a Boolean function by using K-map $F(x, y, z) = \sum (0, 2, 4, 5, 6)$	07
Q.3	(a) Draw a block diagram of 4 to 1 line multiplexer and give functional table.	03
	(b) Differentiate combinational logic circuit and sequential logic circuit.	04
	(c) Design a half adder combinational circuit with diagram and truth table.	07
OR		
Q.3	(a) Draw the block diagram of full adder with two half adders and an OR gate	03
	(b) Describe decoder combinational circuit briefly.	04
	(c) Describe the Magnitude comparator.	07
Q.4	(a) Explain synchronous clocked sequential circuit.	03
	(b) Explain latches and flip- flop briefly.	04
	(c) Describe SR flip flop with circuit diagram.	07
OR		
Q.4	(a) Explain excitation table.	03
	(b) Describe concept of master slave Flip Flop.	04
	(c) Describe D- Flip Flop with necessary circuits.	07
Q.5	(a) Draw a block diagram and timing diagram of serial transfer from register A to register B.	03
	(b) Explain serial in serial out shift register.	04
	(c) Explain classification and characteristics of memories.	07

OR

- | | | |
|------------|--|-----------|
| Q.5 | (a) Explain Random Access Memory (RAM). | 03 |
| | (b) Describe magnetic and optical storage. | 04 |
| | (c) Describe 4-bit ripple counter with figures. | 07 |
